

28/3/2017

AL:daerey...

Et 342

2015/3/16

A W G American weight guide
text book

power system Analysis
by Hadi - scardat

+ Stevenson

1. parameters of a head line

2. Line models

CMIL $\frac{1}{1000 \text{ in}}$

- Φ Complex power flow.

3. Line Compensation.


1 inch = 254

4. Cables

(R, L, C, G)

* ① Conductance: (G) :-

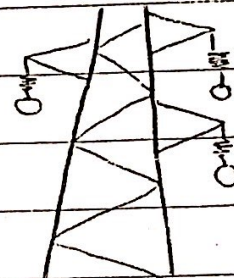① Leakage Current (power loss)
تضيق لما يكون في (توسيع على الحار)



② Corona :- (losses)

bundle

$I^2 R$ Corona loss + leakage

والتي تسمى (G) حصة لأن تأثيرها صغير


omhs/ft at 20 C and Rac, 60-HZ=0.0951 ohms/ft at 50 C. Assuming 1.6% increase due to spiraling. a- Verify Rdc at 20C. b- How much increase in R due to skin effect.

111300 cmil has Rdc=0.0155 E-3



inductance (L) :-

inductance of a single conductor

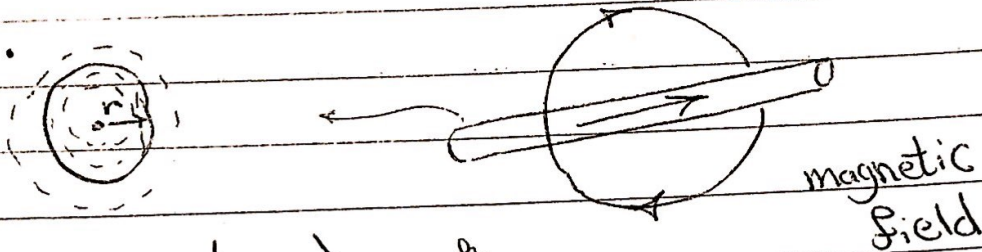


$$L = \frac{\lambda}{I}$$

For non-magnetic material $L = \frac{\lambda}{I} \text{ H} \rightarrow \textcircled{1}$

i induced voltage

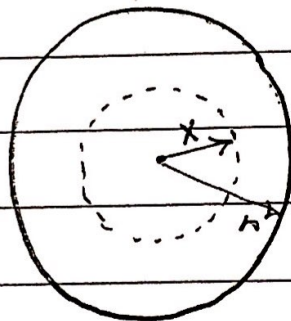$\lambda \equiv$ total flux linkages (web-turn)



$$\int_0^{2\pi x} H_x dl = I \rightarrow \textcircled{2}$$

$H_x =$ magnetic field intensity

شدة المجال المغناطيسي

$$H_x = \frac{I_x}{2\pi x} \rightarrow (3)$$

$$(d)^{16} (2d)^6 (k)^2$$



I_x = Current enclosed at Radius (x)

internal inductance (L_{int}) :-

For uniform Current distribution

$$\frac{I}{\pi r^2} = \frac{I_x}{\pi x^2} \rightarrow (4)$$

(4) into (3) for I_x :-

$$H_x = \frac{1}{2\pi x} \cdot \frac{I \cdot \pi x^2}{\pi r^2} = \frac{x I}{2\pi r^2} \rightarrow (5)$$


For non-magnetic Material :-

$$B_x = \mu_0 H_x$$

$$B_x = \frac{x I}{2\pi r^2} \mu_0 \rightarrow (6)$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$
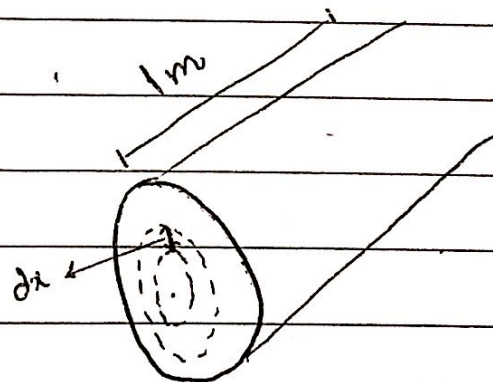
$$d\phi_x = B_x \cdot \text{Area} \cdot 1$$



$$d\phi_x = \frac{x I}{2\pi r^2} \mu_0 dx \rightarrow (7)$$

* note:- Only a fraction $\frac{\pi x^2}{\pi r^2}$ of a total Current is linked by the flux $d\lambda_x = \left(\frac{x^2}{r^2}\right) d\Phi_x$

$$\frac{xI}{2\pi r^2} \mu_0 \quad d\lambda_x = \left(\frac{x^2}{r^2}\right) \frac{xI \mu_0}{2\pi r^2} dx$$

total Flux linkages

$$\lambda_{int} = \int_0^r \frac{\mu_0 I x^3}{2\pi r^4} dx = \frac{\mu_0 I}{2\pi r^4} \left[\frac{x^4}{4} \right]_0^r$$

$$\lambda_{int} = \frac{\mu_0 I}{8\pi} \text{ web/m}$$

$$\therefore L_{int} = \frac{\lambda_{int}}{I} = \frac{\mu_0}{8\pi} = \frac{4\pi \times 10^{-7}}{8\pi}$$

$$L_{int} = \frac{1}{2} \times 10^{-7} \text{ H/m} \rightarrow //$$

the internal inductance of the Conductor is independent of the Conductor Radius (r).


* inductance due to external flux linkages (L_{ext})

from (3)

$$H_x = \frac{I}{2\pi x}$$

$$B_x = \mu_0 H_x = \mu_0 \frac{I}{2\pi x}$$

$$x > r$$

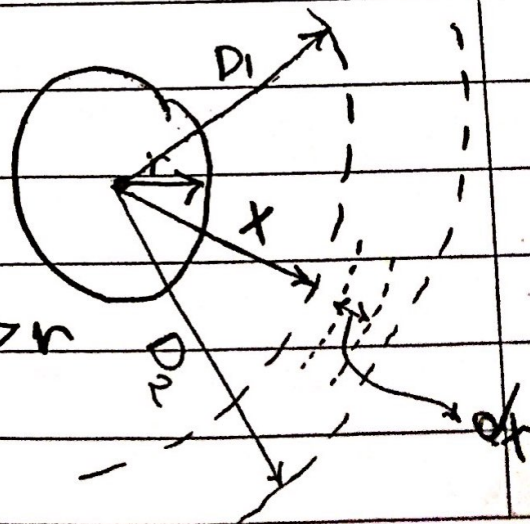

all Current (I) is linked by the flux


$$d\lambda_x = d\phi_x$$

$$= B_x dx = \frac{\mu_0 I}{2\pi x} dx$$

$$\lambda_x = \frac{\mu_0 I}{2\pi} \int_{D_1}^{D_2} \frac{1}{x} dx = 2 \times 10^{-7} \ln \frac{D_2}{D_1} \text{ web/m}$$

$$L_{ext} = 2 \times 10^{-7} \ln \frac{D_2}{D_1} \text{ H/m} \quad \#$$

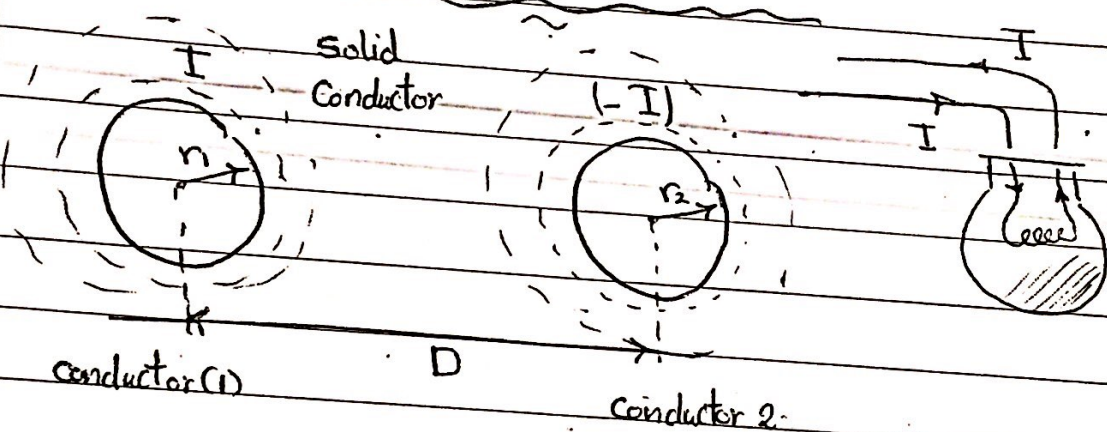inductance of a single-Phase Line :- 2015 / 3 / 19



cond # 1

$$L_{int} = \frac{1}{2} \times 10^{-7} \text{ H/m}$$

$$L_{ext} = 2 \times 10^{-7} \ln \frac{D_2}{D_1} = 2 \times 10^{-7} \ln \frac{D_2}{r_1}$$

$$L_1 = L_{int} + L_{ext} = \frac{1}{2} \times 10^{-7} + 2 \times 10^{-7} \ln \frac{D_2}{r_1}$$

$$= 2 \times 10^{-7} \left(\frac{1}{4} + \ln \frac{D_2}{r_1} \right)$$

$$= 2 \times 10^{-7} \left(\ln e^{1/4} + \ln \frac{1}{r_1} + \ln \frac{D_2}{1} \right)$$

$$= 2 \times 10^{-7} \left(\ln \frac{1}{r_1 e^{-1/4}} + \ln \frac{D}{r_1} \right)$$

$$r_1' = r_1 \cdot e^{-1/4} = 0.7788 r_1$$

$$L_1 = 2 \times 10^{-7} \ln \frac{D}{r_1'} \text{ H/m}$$

Cond # 2

$$L_2 = 2 \times 10^{-7} \ln \frac{D}{r_2'}$$

if $r_1 = r_2 = r$

$$L_1 = L_2 = 2 \times 10^{-7} \ln \frac{D}{r_1'} \text{ H/m}$$

$$L_1 = L_2 = L = 0.2 \ln \frac{D}{r_1'} \text{ mH/km}$$

$$r_1' = r e^{-1/4} \equiv \text{self geometrical mean distance (Radius)} \\ \equiv \text{GMR} \quad D_s$$

$$L = 0.2 \ln \frac{D}{r_1'} \text{ (mH/km)} \quad \text{in for One Conductor}$$

\therefore For the Complete Circuit of single Phase line

$$L = L_1 + L_2 = 2L$$

$$L = 4 \times 10^{-7} \ln \frac{D}{r_1'} \text{ (H/m)}$$


$$L = 0.4 \times 10^{-7} \ln \frac{D}{r_1'} \text{ (mH/km)}$$

* Flux Linkages in terms of self and mutual inductance...

$$\lambda_1 = L_{11} I_1 + L_{12} I_2$$


$$\lambda_2 = L_{21} I_1 + L_{22} I_2$$

$$I_1 = -I_2 \rightarrow I_2 = -I_1$$

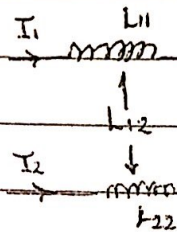

$$\lambda_1 = (L_{11} - L_{12}) I_1$$

$$\lambda_2 = (-L_{21} + L_{22}) I_2$$

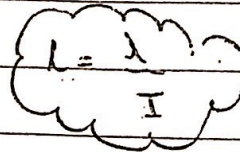

$$L_1 = \frac{\lambda_1}{I_1} = \overset{\text{mutual}}{L_{11} - L_{12}} = 2 \times 10^{-7} \ln \frac{D}{r_1} = 2 \times 10^{-7} \left(\ln D + \ln \frac{1}{r_1} \right)$$

$$L_2 = \frac{\lambda_2}{I_2} = -L_{21} + L_{22}$$

self

$$L_{11} = 2 \times 10^{-7} \ln \frac{1}{r_1}$$

$$L_{12} = 2 \times 10^{-7} \ln \frac{1}{D}$$

$$L_2 = \frac{\lambda_2}{I_2} = -L_{21} + L_{22} = 2 \times 10^{-7} \ln \frac{D}{r_2}$$


$$L_{22} = 2 \times 10^{-7} \ln \frac{1}{r_2}$$

$$L_{21} - L_{12} = 2 \times 10^{-7} \ln \frac{1}{D}$$

for (n) conductor I_1, I_2, \dots, I_n
 such that $I_1 + I_2 + I_3 + \dots + I_n = 0$

for conductor i :-
 $\lambda_i = L_{ii} I_i + \sum_{j=1}^n L_{ij} I_j \quad i \neq j$
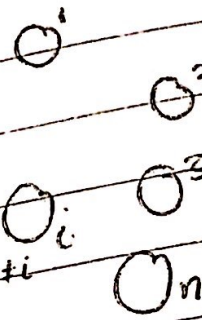
$$\text{or } \lambda_i = 2 \times 10^{-7} \left(I_i \ln \frac{1}{r_i} + \sum_{j=1}^n I_j \ln \frac{1}{D_{ij}} \right) \quad j \neq i$$



* inductance of Three Phase transmission lines :-

① symmetrical spacing


في الجبهة غير موجودة أو دائرية

for 1m of the line

we Assume balance 3-Phase

Currents :-

$$I_a + I_b + I_c = 0$$

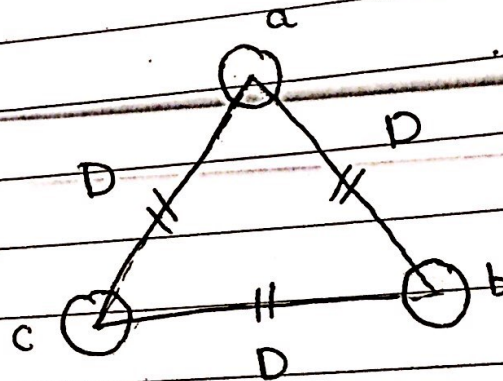

Flux Linkage

~~$$\lambda_a = 2 \times 10^{-7} \left(I_a \ln \frac{1}{r_i} + I_b \ln \frac{1}{D} + I_c \ln \frac{1}{D} \right)$$~~

* Single

$$L = L_a + L_b$$



* Three Phase

$$L = L_a = L_b = L_c$$



Flux Linkage

$$\lambda_a = 2 \times 10^{-7} \left(I_a \ln \frac{1}{r_i} + I_b \ln \frac{1}{D} + I_c \ln \frac{1}{D} \right)$$

$$I_b + I_c = -I_a$$

$$\lambda_a = 2 \times 10^{-7} \left(I_a \ln \frac{1}{r'} - I_a \ln \frac{1}{D} \right)$$

$$\ln \frac{1}{D} (I_a + I_b) = -I_a \ln \frac{1}{D}$$

$$\lambda_a = 2 \times 10^{-7} I_a \ln \frac{D}{r'} \quad \text{H/m} \rightarrow \#$$

$$\therefore \lambda_b = 2 \times 10^{-7} I_b \ln \frac{D}{r'}$$

$$\lambda_c = 2 \times 10^{-7} I_c \ln \frac{D}{r'}$$

$$L_a = \frac{\lambda_a}{I_a} = 2 \times 10^{-7} \ln \frac{D}{r'} \quad \text{H/m}$$

$\text{GMR} \rightarrow \begin{cases} \text{Solid} = r e^{-1/4} \\ \text{Strand} = \dots \end{cases}$


$$L = L_a = L_b = L_c = \text{H/m/phase}$$

$$L = 0.2 \ln \frac{D}{r'} \quad \text{mH/km/phase}$$

* For Solid Conductor $r' = 0.7788 r$

* // Strand // \rightarrow use table (GMR) or (Ds)

② ^{non-}symmetrical spacing :-

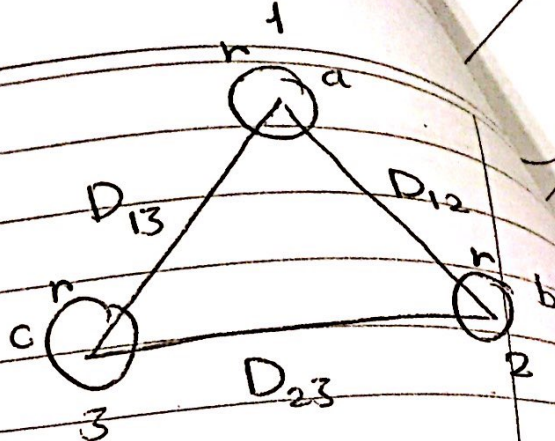

$$\lambda = 2 \times 10^{-7} \left(I_i \ln \frac{1}{r'} + \sum I_j \ln \frac{1}{D_{ij}} \right)$$


$$\lambda_a = 2 \times 10^{-7} \left(I_a \ln \frac{1}{r'} + I_b \ln \frac{1}{D_{12}} + I_c \ln \frac{1}{D_{13}} \right)$$

$$\lambda_b = 2 \times 10^{-7} \left(I_a \ln \frac{1}{D_{12}} + I_b \ln \frac{1}{r'} + I_c \ln \frac{1}{D_{23}} \right)$$

$$\lambda_c = 2 \times 10^{-7} \left(I_a \ln \frac{1}{D_{13}} + I_b \ln \frac{1}{D_{23}} + I_c \ln \frac{1}{r'} \right)$$

$$I_a \angle 120^\circ = I_c$$

$$I_a \angle 240^\circ = I_b$$

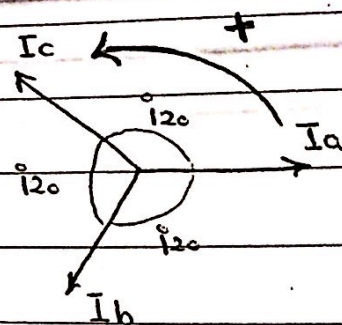

$$a = 1 \angle 120^\circ, \quad a^2 = 1 \angle 240^\circ$$

$$a^3 = 1 \angle 360^\circ$$

$$\lambda_a = 2 \times 10^{-7} \left(I_a \ln \frac{1}{r'} + I_a a^2 \ln \frac{1}{D_{12}} + a I_a \ln \frac{1}{D_{13}} \right)$$

$$L_a = \frac{\lambda_a}{I_a} = 2 \times 10^{-7} \left(\ln \frac{1}{r'} + a^2 \ln \frac{1}{D_{12}} + a \ln \frac{1}{D_{13}} \right)$$

$$a + a^2 = -1$$

$$\angle 120^\circ + \angle 240^\circ = -1$$

28/3/2017

$$L_a \neq L_b \neq L_c$$

$$L_{avg} = \frac{L_a + L_b + L_c}{3} = \frac{2 \times 10^{-7}}{3} \left(3 \ln \frac{1}{r'} - \ln \frac{1}{D_{12}} - \ln \frac{1}{D_{13}} - \ln \frac{1}{D_{23}} \right)$$

$$\frac{1}{3} \ln \frac{1}{D} = \ln \left(\frac{1}{D} \right)^{1/3} = \ln \frac{1}{D^{1/3}}$$

$$L_{avg} = 2 \times 10^{-7} \left(\ln \frac{1}{r'} - \ln \frac{1}{(D_{12} D_{23} D_{13})^{1/3}} \right)$$

$$L_{avg} = 2 \times 10^{-7} \ln \frac{(D_{12} D_{23} D_{13})^{1/3}}{r'}$$

$$L_{avg} = 2 \times 10^{-7} \ln \frac{GMD}{r'} \quad H/m$$

$$GMD = \sqrt[3]{D_{12} D_{23} D_{13}} \quad \text{"Geometrical mean distance"}$$

$$L = 0.2 \ln \frac{GMD}{r'} \quad mH/km/phase$$

$$L = 0.2 \ln \frac{GMD}{GMR}$$

Ex # 1 :-


① Single-Phase Line :-

The Conductor of a single Phase line, 60 Hz, is a solid solid round aluminum Conductor,

Spacing 3m

Dia = 0.412 cm

D = 3m

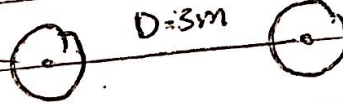

Determine the inductance of the line in (mH/mile) How much of this inductance is due to internal flux-linkage neglect skin-effect.

solution

$$L = 2 \times 10^{-7} \ln \frac{D}{r'} \quad (\text{H/m})$$

$$r = \frac{0.412 \text{ cm}}{2} = 0.206 \text{ cm}$$

$$r' = e^{-1/4} \cdot r = 0.206 \times 0.7788 \text{ cm}$$

$$L = 2 \times \left[2 \times 10^{-7} \ln \frac{300 \text{ cm}}{0.206 \times 0.7788 \text{ cm}} \cdot \frac{\text{H}}{\text{m}} \cdot \left(\frac{10^3 \text{ mH}}{1 \text{ H}} \right) \left(\frac{1609 \text{ m}}{1 \text{ mile}} \right) \right]$$


$$L = 4.85 \text{ mH/mile}$$

$$L_{in} = 2 \times \left(\frac{1}{2} \times 10^{-7} \times 10^3 \times 1609 \text{ mH/mile} \right)$$

$$L_{in} = 0.16 \text{ mH/mile}$$

Ex #2 3 phase Line

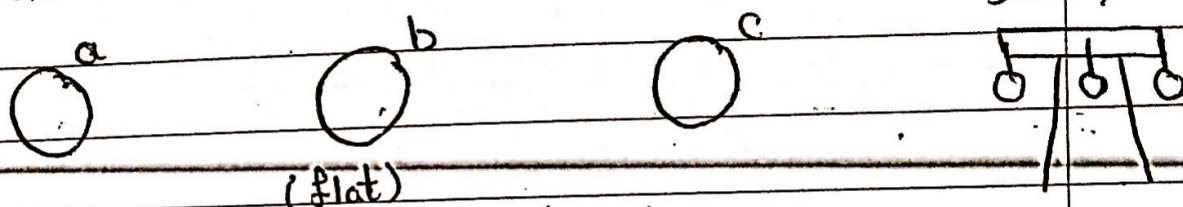A 500-kV 3-phase (ph) transposed Line.
Composed of One (ACSR) (1272000 cmil)




* (45/7) → bittorn Conductor/ph

* horizontal spacing

* Diam = 1.345 inch

* GMR = 0.5328 inch

Calculate the inductance/ph/km.

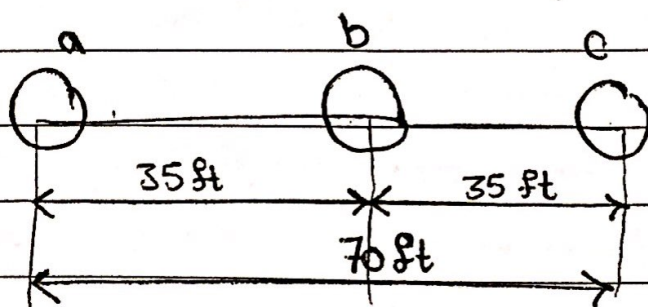

Solution

$$L = 2 \times 10^{-7} \ln \frac{GMD}{GMR}$$


$$GMD = \sqrt[3]{D_{12} \cdot D_{13} \cdot D_{23}}$$

$$GMD = \sqrt[3]{(35)(35)(70)} = 44.097 \text{ ft}$$





$$L = 2 \times 10^{-7} \ln \frac{44.097 \text{ ft} \times 12 \text{ inch}}{0.5328 \text{ inch}}$$

$$L = 0.2 \ln \frac{44.097 \text{ ft} \times 12 \text{ inch}}{0.5328 \text{ inch}} = 1.38 \text{ mH/km}$$


* inductance of Composite Conductors :-

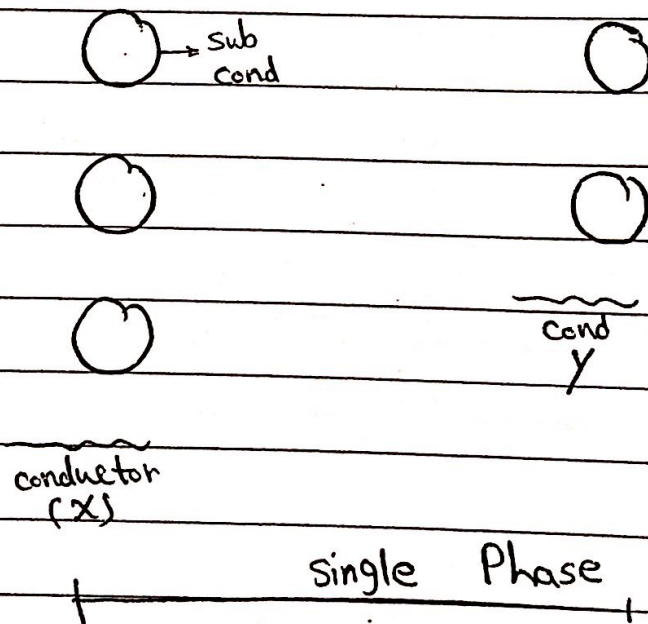

Sub
Cond

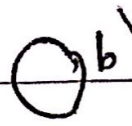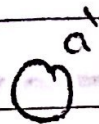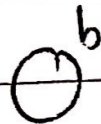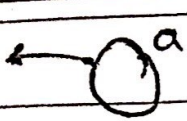


$$I_t = \frac{I}{n}$$

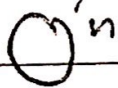

X

$$-I_t = -\frac{I}{m}$$

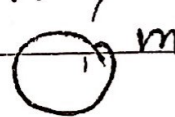

Y

$$\lambda_i = 2 \times 10^{-7} \left(I_i \ln \frac{1}{r_i'} + \sum_{j=1}^n I_j \ln \frac{1}{D_{ij}} \right) \quad j \neq i$$

$$\lambda_a = 2 \times 10^{-7} \left(\frac{I}{n} \ln \frac{1}{r_a'} + \frac{I}{n} \ln \frac{1}{D_{ab}} + \frac{I}{n} \ln \frac{1}{D_{ac}} + \dots + \frac{I}{n} \ln \frac{1}{D_{an}} \right) - 2 \times 10^{-7} \left(\frac{I}{m} \ln \frac{1}{D_{aa'}} + \frac{I}{m} \ln \frac{1}{D_{ab'}} + \dots + \frac{I}{m} \ln \frac{1}{D_{am'}} \right)$$

$$\lambda_a = 2 \times 10^{-7} I \ln \left[\frac{\sqrt[n]{D_{aa'} D_{ab'} D_{ac'} \dots D_{am'}}}{\sqrt[n]{r_a' D_{ab} D_{ac} \dots D_{an}}} \right]$$

$$L_a = \frac{\lambda_a}{I/n} \rightarrow T_a = \frac{I}{n}$$

$$L_a = n 2 \times 10^{-7} \ln \frac{\sqrt[n]{D_{aa'} \cdot D}}{\sqrt[n]{\dots}}$$

$$L_{xn} = \frac{\lambda}{I/n} = n \times 10^{-7} \ln \frac{\sqrt[m]{D_{na} D_{nb} \dots D_{nm}}}{\sqrt[n]{r_x D_{na} D_{nb} \dots}}$$

$$L_{avg} = \frac{L_a + L_b + \dots + L_n}{n}$$

$$\therefore L_x = \frac{L_{avg}}{n}$$

$$L_x = \frac{L_a + L_b + \dots + L_n}{n^2}$$

هذا خطا
لانهم متوزعات
بشكل (L)
اللي

$$L_x = 2 \times 10^{-7} \ln \frac{GMD}{GMR} \quad H/m$$

هذا كذا
(y, x) ←

$$GMD = \sqrt[mn]{(D_{aa})(D_{ab}) \dots D_{am})(D_{bb} D_{ba} \dots D_{bm})(D_{ca} \dots D_{cn} \dots D_{nn})}$$


$$GMR_x = \sqrt[n^2]{(D_{aa} D_{ab} D_{ac} \dots D_{an})(D_{ba} D_{bb} D_{bc} \dots D_{bn})(D_{ca} D_{cb} D_{cc} \dots D_{cn})}$$

$$GMR_y = \sqrt[m^2]{(D_{aa} D_{ab} D_{am})(D_{ba} D_{bb} \dots D_{bm}) \dots}$$

$$D_{aa} = D_{bb} = D_{cc} = \dots D_{nn} = r'_x$$

$$D_{aa'} = D_{bb'} = D_{cc'} = \dots D_{nn} = r'_y$$

* Transposition

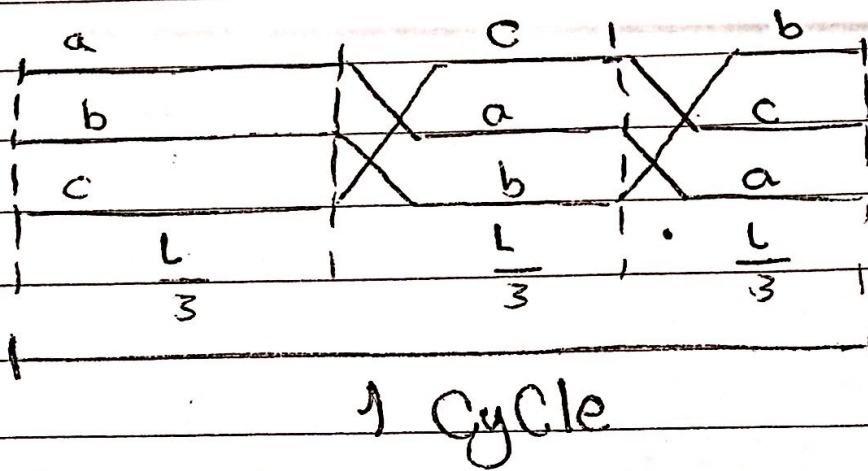

2015 / 3 / 26

* Ex: #1 Composite Conductors

x: solid $r = 0.25 \text{ cm}$

y: solid $r = 0.5 \text{ cm}$

for the single-Phase line
shown, find the inductance
of the line in (H/m) and $(\text{mH})/(\text{mi})$

Solution

$$L_x = 2 \times 10^{-7} \ln \frac{\text{GMD}}{\text{GMR}_x}$$

$$L_y = 2 \times 10^{-7} \ln \frac{\text{GMD}}{\text{GMR}_y}$$

$$L_{in} = L_x + L_y$$


$$D_{ad} = 9 \text{ m} = D_{be}$$

$$D_{ae} = \sqrt{9^2 + 6^2} = 3\sqrt{13} = D_{bd} = D_{ce}$$

$$D_{cd} = \sqrt{9^2 + 12^2} = 15 \text{ cm}$$

$$\text{GMD} = \sqrt[6]{D_{ad} \cdot D_{ae} \cdot D_{bd} \cdot D_{be} \cdot D_{cd} \cdot D_{ce}} = 10.743 \text{ m}$$
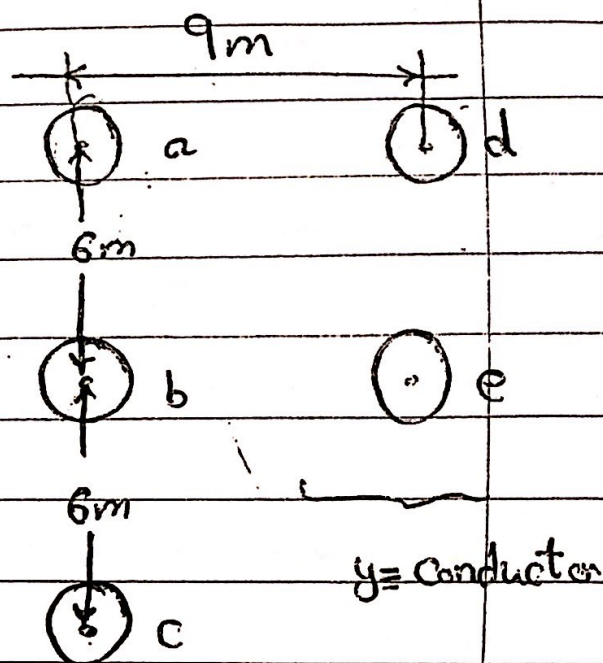
$$\text{GMR}_x = \sqrt[9]{(D_{aa} \cdot D_{ab} \cdot D_{ac})(D_{ba} \cdot D_{bb} \cdot D_{bc})(D_{ca} \cdot D_{cb} \cdot D_{cc})}$$



x = conductor

y = conductor

$$= \sqrt[9]{(r')^3 (6)^4 (12)^2} = \sqrt[9]{(0.7788 [0.25 \times 10^{-2}])^3 (6)^4 (12)^2}$$

$$GMR_x = 0.481 \text{ m}$$

$$GMR_y = \sqrt[4]{D_{dl} D_{de} D_{ed} D_{ee}} = \sqrt[4]{r_y^2 (6)^2}$$

$$= \sqrt[4]{[0.7788 \times (0.5 \times 10^{-2})]^2 (6)^2}$$

$$GMR_y = 0.153 \text{ m}$$

$$(1) L_x = 2 \times 10^{-7} \ln \frac{10.743}{0.481} = 6.212 \times 10^{-7} \text{ H/m}$$

$$L_y = 2 \times 10^{-7} \ln \frac{10.743}{0.153} = 8.503 \times 10^{-7} \text{ H/m}$$

$$(2) L_x = 6.212 \times 10^{-7} \frac{\text{H}}{\text{m}} \cdot \frac{10^3 \text{ mH}}{\text{H}} \cdot \frac{1609 \text{ m}}{\text{mil}} = \text{''} \frac{\text{mH}}{\text{mil}}$$


$$L_y = 8.503 \times 10^{-7} \frac{\text{H}}{\text{m}} \cdot \frac{10^3 \text{ mH}}{\text{H}} \cdot \frac{1609 \text{ m}}{\text{mil}} = \text{''} \frac{\text{mH}}{\text{mil}}$$

$$L = L_x + L_y = 14.715 \times 10^{-7} \text{ H/m}$$

$$L = 14.715 \times 10^{-7} \frac{\text{H}}{\text{m}} \times \frac{10^3 \text{ mH}}{\text{H}} \times \frac{1609 \text{ m}}{\text{mil}} = 2.37 \frac{\text{mH}}{\text{mil}}$$

Ex: #2

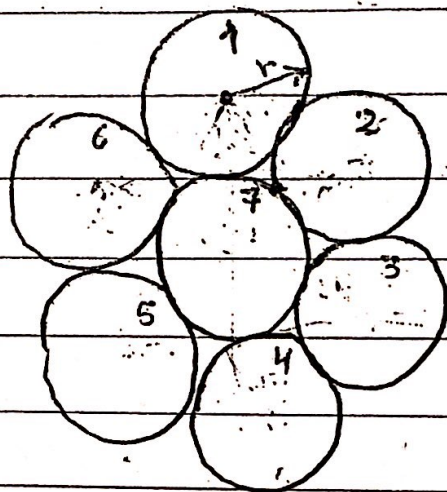A stranded Conductor has (7) strands as shown, each strand has Radius (r) Determine the (GMR) of the Conductor in terms of (r).



$$GMR = \sqrt[49]{(D_{11} D_{12} D_{13} D_{14} D_{15} D_{16} D_{17})^6}$$

$$D_{11} = D_{22} = D_{33} = D_{44} = D_{55} = D_{66} = D_{77} = r' = 0.7788r$$

$$D_{12} = D_{16} = D_{17} = 2r$$

$$D_{13} = \sqrt{D_{14}^2 - D_{34}^2} = \sqrt{(4r^2) - (2r)^2} = \sqrt{(16-4)r^2} = 2\sqrt{3}r$$

$$D_{13} = 2\sqrt{3}r = D_{15}$$


$$D_{14} = 4r$$

$$D_{34} = 2r$$

$$GMR = \sqrt[49]{\left[(0.7788r)(2r)^3 (2\sqrt{3}r)^2 (4r) \right]^6 \left[(0.7788r)(2r)^6 \right]}$$

$$GMR = 2.176r$$

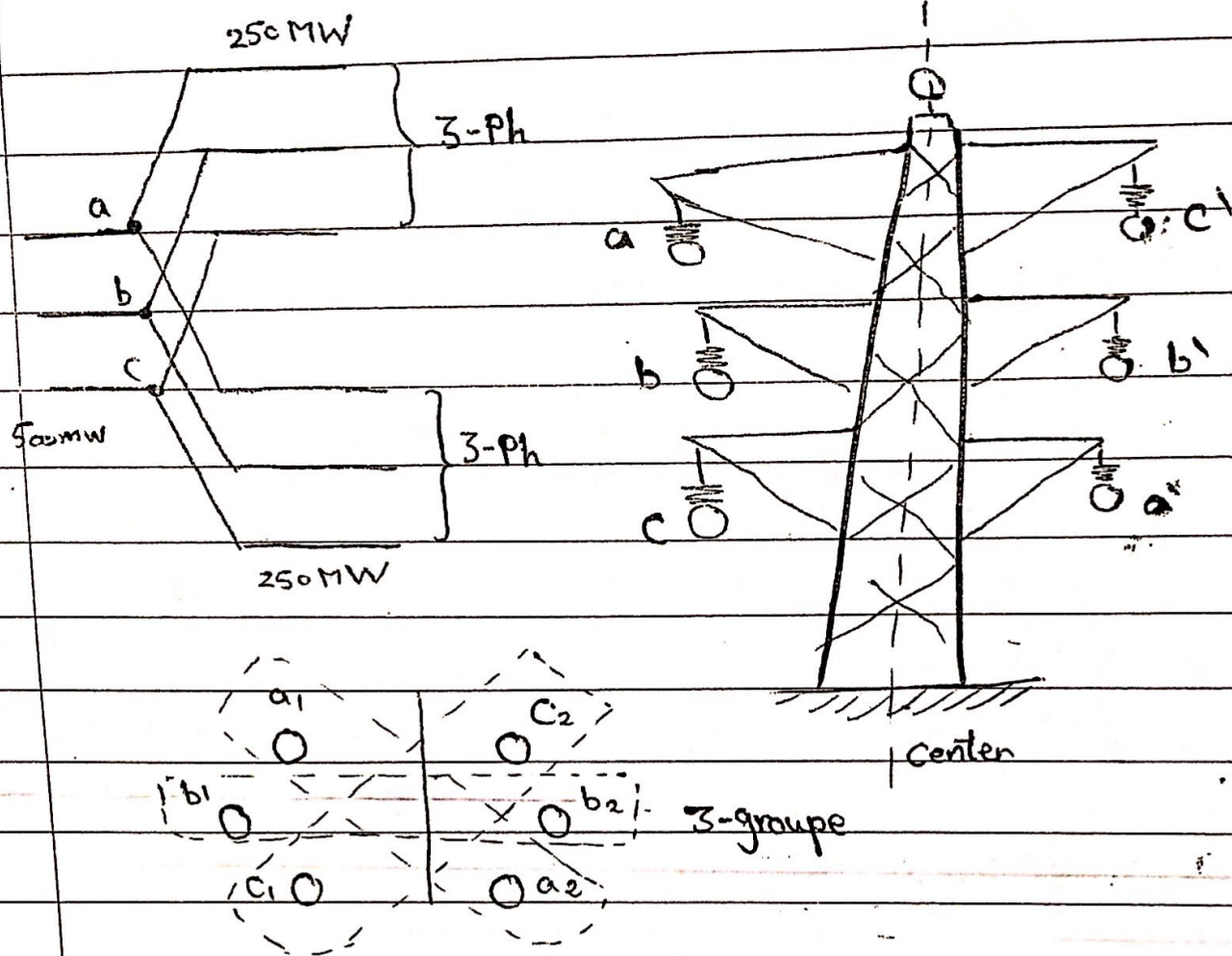inductance of double-Circuit line (3-Phase):



* to find GMD:-

① find (GMD) between any two groups.

$$GMD_{AB} = \sqrt[4]{D_{a_1b_1} D_{a_1b_2} D_{a_2b_1} D_{a_2b_2}}$$

$$GMD_{BC} = \sqrt[4]{D_{b_1c_1} D_{b_1c_2} D_{b_2c_1} D_{b_2c_2}}$$

$$GMD_{AC} = \sqrt[4]{D_{a_1c_1} D_{a_1c_2} D_{a_2c_1} D_{a_2c_2}}$$

$$GMD_{equivalent} = \sqrt[3]{(GMD_{AB})(GMD_{BC})(GMD_{AC})}$$

② Find GMR

$$GMR_A = \sqrt[4]{D_{a1}a_1 D_{a1}a_2 D_{a2}a_1 D_{a2}a_2}$$

$$r' = D_{a1}a_1 = D_{a2}a_2 = D_s$$

$$GMR_A = \sqrt[4]{(D_s D_{a1}a_2)^2} = \sqrt{D_s D_{a1}a_2}$$

$$GMR_A = \sqrt{D_s D_{a1}a_2}$$

$$GMR_B = \sqrt{D_s D_{b1}b_2}$$

$$GMR_C = \sqrt{D_s D_{c1}c_2}$$

$$GMR_{equ} = \sqrt[3]{(GMR_A)(GMR_B)(GMR_C)}$$

③ $L = 2 \times 10^{-7} \ln \frac{GMD_{equ}}{GMR_{equ}} \left(\frac{H}{m} \right)$

* Ex :- #3

inductance of a (3-Ph) Double
(cmil) Circuit line has


(300,000) (26/7) "ostrich"

feet = 1'

inch = 1"

Conductors arranged as shown

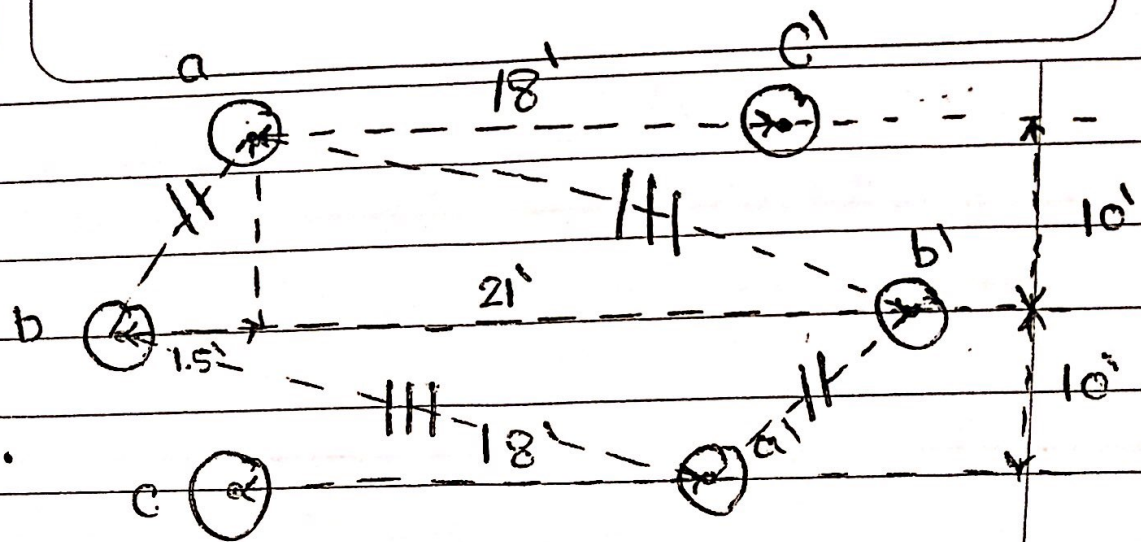Find the (60-Hz) inductive Reactance
of the line



$$GMD_{AB} = \sqrt[4]{(10.1 \times 21.9)^2} = 14.88'$$

$$D_{ab} = D_{a'b'} = \sqrt{1.5^2 + 10^2} = 10.1'$$

$$D_{ab'} = D_{a'b} = \sqrt{19.5^2 + 10^2} = 21.9'$$

$$GMD_{BC} = GMD_{AB}$$

$$GMD_{AC} = \sqrt[4]{D_{ac} \cdot D_{ac'} \cdot D_{a'c} \cdot D_{a'c'}} = 18.97'$$

$$GMR_A = \sqrt{D_s \cdot D_{aa'}} = \sqrt{0.0229 \times 26.9} = 0.785'$$

$$GMR_B = \sqrt{0.0229 \times 21} = 0.693'$$

$$GMR_C = 0.785'$$

$$GMR_{eq} = \sqrt[3]{(0.785)^2 \times 0.693} = 0.753'$$

$$L = 2 \times 10^{-7} \ln \frac{16.1}{0.753} = 6.13 \times 10^{-7} \left(\frac{H}{m} \right)$$

$$X_L = \omega L = 2\pi f L$$

$$= 2\pi \times (60 \text{ Hz}) (6.13 \times 10^{-7} \times 10^3) = 0.23 \text{ } \cancel{\text{km}}^{\Omega}$$

* Bundle Conductors :-

$$L = 0.2 \ln \frac{GMD}{GMR} \text{ mH/km}$$



$$n = 2$$

$$GMR(b) = \sqrt[4]{D_{aa} D_{aa_1} D_{a_1a} D_{a_1a_1}}$$

$$D_s = D_{aa} \quad D_s = D_{a_1a_1}$$

$$= \sqrt[4]{D_s^2 D_{a_1a}^2}$$




$$GMR(b) = \sqrt{D_s d}$$

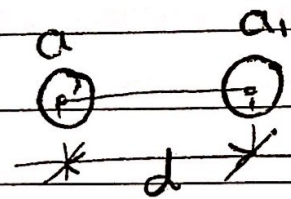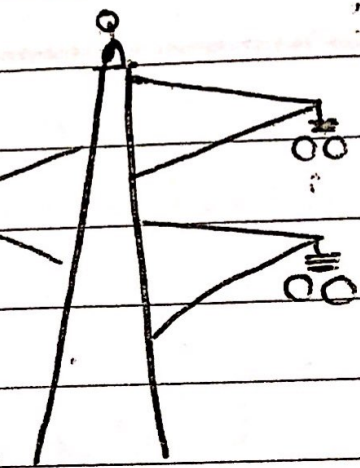

$$GMR(b) = \sqrt[9]{(D_{aa} D_{aa_1} D_{a_1a} D_{a_1a_1})^3}$$



$$= \sqrt[9]{(D_s)^3} = \sqrt[9]{(D_s d)^3}$$

$$= \sqrt[3]{D_s d^2}$$

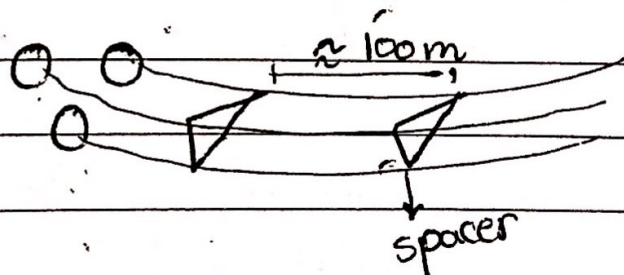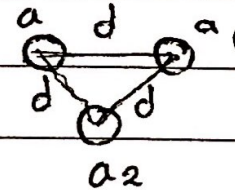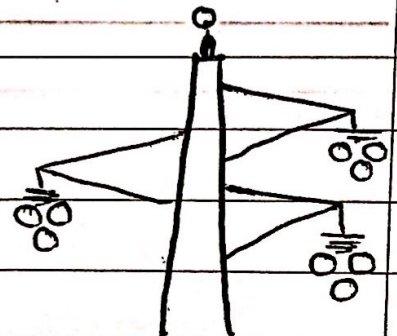


$$GMR(b) = \sqrt[16]{(D_s d (\sqrt{2} d) d)^4}$$

$$GMR(b) = 1.09 \sqrt[4]{D_s d^3}$$

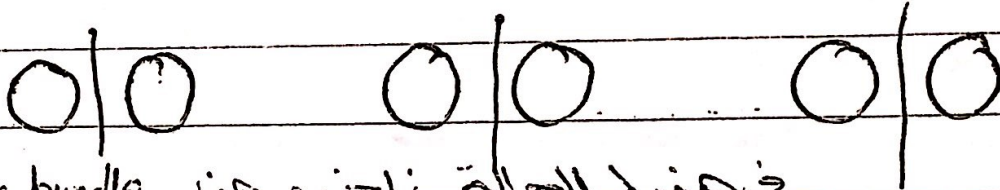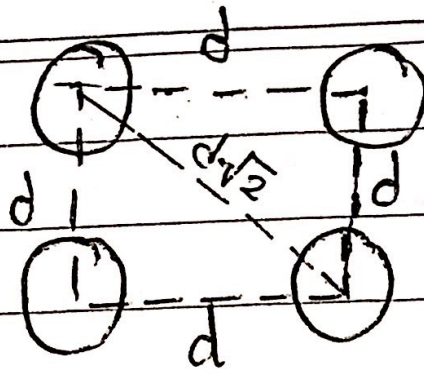

في هذه الحالة نأخذ من Center bundle إلى Center bundle وليس من center cond

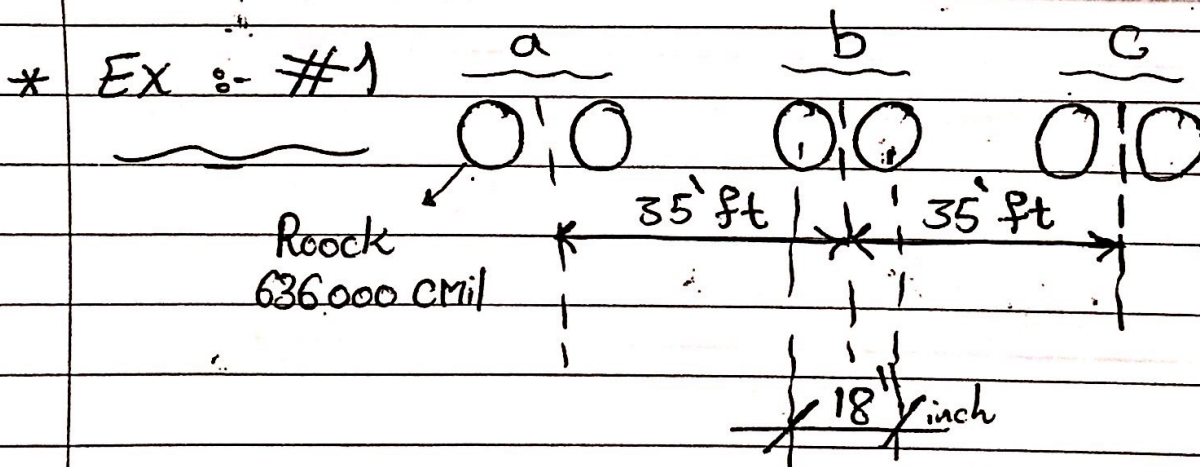قد ترتفع ذللك (power) $P \propto \frac{1}{x}$



$$GMR = 0.3924 \text{ inch}$$

$$GMR(b) = \sqrt{0.3924 \times 18} = 2.657 \text{ inch}$$

$$GMR(b) = \frac{2.657}{12} = 0.2214 \text{ ft}$$

$$GMD = \sqrt[3]{35 \times 35 \times 70} = 44.097$$

$$L = 0.2 \ln \frac{44.097}{0.22147} = 1.0588 \text{ mH/km}$$

$$\therefore \% \text{ decrease in } L = 23.3\%$$


Capacitance (C)

$$Y = G + jB \text{ (S)}$$

$$= G + j\omega C$$

$$G = \frac{1}{R}$$

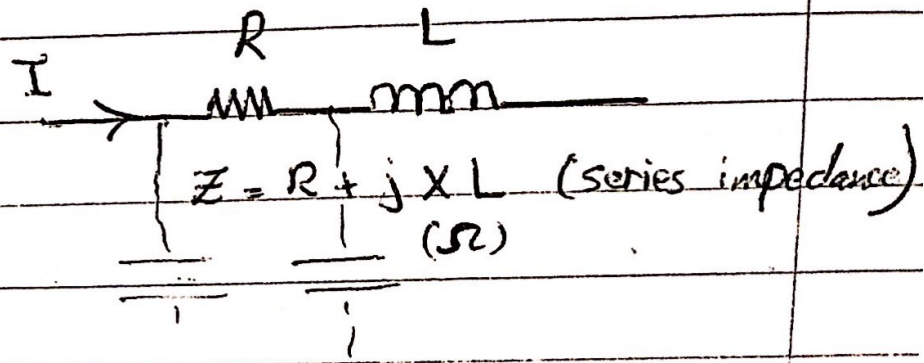
$$Y = j\omega C \text{ (shunt admittance)}$$



ground

$$C = \frac{q}{V}$$

$$\phi = Q$$

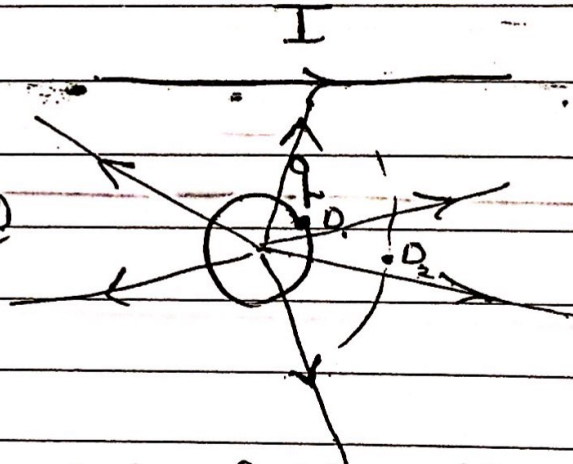

Electric field lines.

$$E = \frac{D}{\epsilon_0}$$

E = electric field intensity

D = flux density

ϵ_0 = permittivity free space

$$8.85 \times 10^{-12}$$

$$D = \frac{q}{A} = \frac{q}{(2\pi r)(1)} = \frac{q}{2}$$


$$E = \frac{q}{2\pi(x)\epsilon_0}$$

$$V_{12} = \int_{D_1}^{D_2} E \cdot dx = \int_{D_1}^{D_2} \frac{q}{2\pi\epsilon_0 x} dx = \frac{q}{2\pi\epsilon_0} \ln \frac{D_2}{D_1}$$

x عافیه

Capacitance of single-phase lines:-
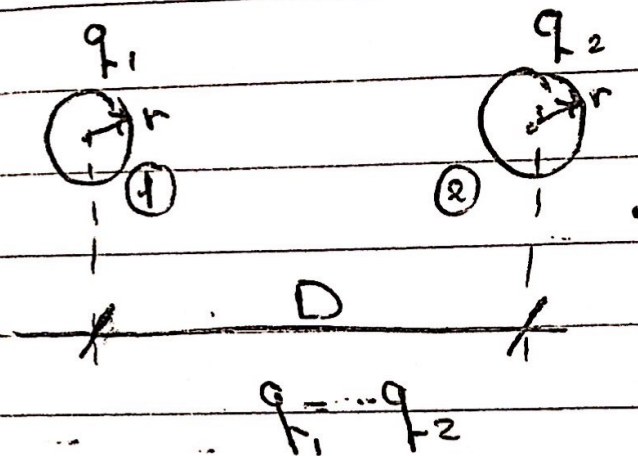
$$V_{12} = \frac{q}{2\pi\epsilon_0} \ln \frac{D}{D_1}$$



For (1m) of the line:-

$$D \gg r$$

* Conductor # 1 :- (alone)

$$V_{12}(q_1) = V_{12} = \frac{q_1}{2\pi\epsilon_0} \ln \frac{D}{r} \rightarrow (q_1)$$

* Conductor # 2 :- (alone)

$$V_{21}(q_2) = \frac{q_2}{2\pi\epsilon_0} \ln \frac{D}{r}$$

$$V_{12}(q_2) = -V_{21}(q_2)$$

$$V_{12}(q_2) = \frac{q_2}{2\pi\epsilon_0} \ln \frac{r}{D}$$

using source position :-

$$V_{12} = V_{12}(q_1) + V_{12}(q_2)$$


$$= \frac{q_1}{2\pi\epsilon_0} \ln \frac{D}{r} + \frac{q_2}{2\pi\epsilon_0} \ln \frac{r}{D}$$

let $q_1 = -q_2 = q$

$$V_{12} = \frac{q}{2\pi\epsilon_0} \ln \frac{D}{r}$$

$$C_{12} = \frac{q}{V_{12}}$$
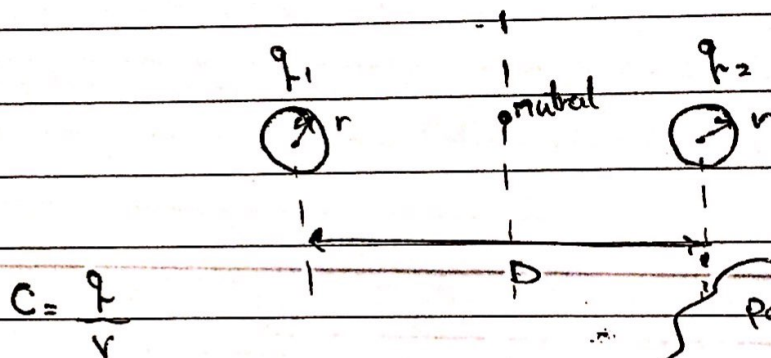
$$\Rightarrow C_{12} = \frac{\pi\epsilon_0}{\ln \frac{D}{r}} \text{ F/m}$$



$$C_{n1} V_{12} = C_{12} V_{12}$$

$$C_n \frac{1}{2} V_{12} = C_{12} V_{12}$$

$$C_n = 2 C_{12}$$

Power :-
and neutral is in the
of line of line in
conduc of Conduc

$$C_n = \frac{2\pi\epsilon_0}{\ln D/r} \text{ F/m}$$

$$= \frac{2 \times \pi \times 8.85 \times 10^{-12} \times 10^6 \text{ F}}{1 \text{ F}} \cdot \frac{10^3 \text{ m}}{1 \text{ Km}}$$

$$C_n = C_o = \frac{0.0556}{\ln D/r} \text{ MF/Km}$$

note :-

- ① for L, $r' = e^{-1/4}$
- ② for C, $r = \text{radius of Conduc}$

* Potential difference in multi Conductor Configuration :-

- (n) parallel conductance


- We Assume $q_1 + q_2 + \dots + q_n = 0$

$$V_{ij} = \frac{1}{2\pi\epsilon_0} \sum_{k=1}^n \frac{q_k \ln \frac{D_{kj}}{r_k}}{D_{kj}}$$

$$V_{12} = \frac{1}{2\pi\epsilon_0} \left(\frac{q_1 \ln \frac{D}{r_1}}{r_1} + \frac{q_2 \ln \frac{r_2}{D}}{r_2} \right) \checkmark$$

* Capacitance of 3-Phase Line :-

① non-symmetrical

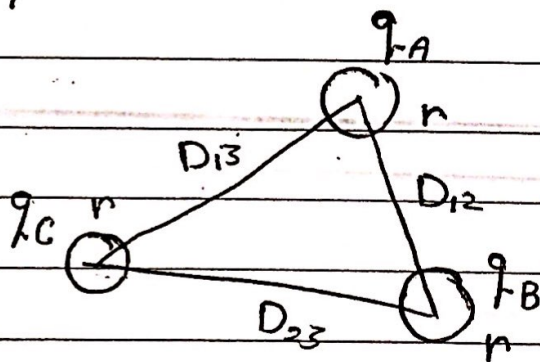


① For (1m) of the (3-Ph) line

$$q_A + q_B + q_C = 0$$

② Ground Effect is neglected.

③ Assume transposition.

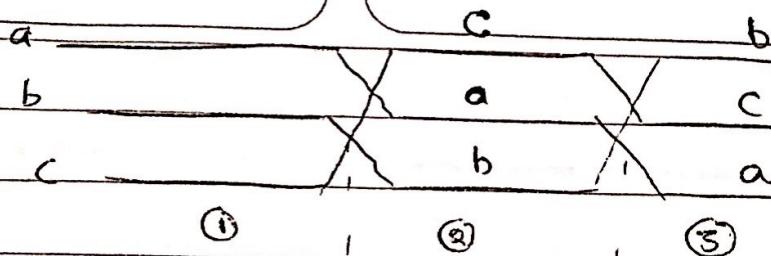

(Transposition Line).

Calculate V_{AB} ? stage (1)

$$V_{AB} = \frac{1}{2\pi\epsilon_0} \left[q_A \ln \frac{D_{12}}{r} + q_B \ln \frac{r}{D_{12}} + q_C \ln \frac{D_{23}}{D_{13}} \right]$$

V_{AB} stage (2)

$$V_{AB} = \frac{1}{2\pi\epsilon_0} \left[q_A \ln \frac{D_{23}}{r} + q_B \ln \frac{r}{D_{23}} + q_C \ln \frac{D_{13}}{D_{12}} \right]$$

V_{AB} stage (3)

$$V_{AB} = \frac{1}{2\pi\epsilon_0} \left[q_A \ln \frac{D_{13}}{r} + q_B \ln \frac{r}{D_{13}} + q_C \ln \frac{D_{12}}{D_{23}} \right]$$

take Average Value (V_{AB}).

$$V_{AB(\text{avg})} = \frac{1}{3(2\pi\epsilon_0)} \left(q_A \ln \frac{D_{12} D_{23} D_{13}}{r^3} + q_B \ln \frac{r^3}{D_{12} D_{23} D_{13}} + q_C \ln \frac{D_{13} D_{12} D_{23}}{D_{13} D_{12} D_{23}} \right)$$

Zero

$$V_{AB(\text{Avg})} = \frac{1}{2\pi\epsilon_0} \left(q_A \ln \frac{\sqrt[3]{D_{12} D_{23} D_{13}}}{r} + q_B \ln \frac{r}{\sqrt[3]{D_{12} D_{13} D_{23}}} \right)$$

$$V_{AB(\text{avg})} = \frac{1}{2\pi\epsilon_0} \left(q_A \ln \frac{\text{GMD}}{r} + q_B \ln \frac{r}{\text{GMD}} \right)$$

similary

$$V_{AC} (\text{avg}) = \frac{1}{2\pi\epsilon_0} \left(q_A \ln \frac{GMD}{r} + q_C \ln \frac{r}{GMD} \right)$$

$$V_{AB} + V_{AC} =$$

$$q_A + q_B + q_C = 0 \quad -q_A = q_B + q_C$$

$$V_{AB} + V_{AC} = \frac{1}{2\pi\epsilon_0} \left[2q_A \ln \frac{GMD}{r} + q_A \ln \frac{GMD}{r} \right]$$

$$V_{AB} + V_{AC} = \frac{1}{2\pi\epsilon_0} \left(3q_A \ln \frac{GMD}{r} \right) \rightarrow *$$

$V_{AC} = V_{An} \angle 0^\circ - V_{An} \angle -240^\circ$
 $V_{AB} + V_{AC} = 2V_{An} \angle 0^\circ - V_{An} \angle -120^\circ - V_{An} \angle -240^\circ$
 $= 3V_{An}$

$V_{AB} = V_{An} \angle 0^\circ + V_{An} \angle 120^\circ$
 $V_{AB} = V_{An} \angle 0^\circ + V_{Bn} \angle 0^\circ$

For Balance (3-Ph) voltages :

$$\frac{3}{V_{An}} = \frac{3q_A}{2\pi\epsilon_0} \ln \frac{GMD}{r}$$

$$C_{an} = \frac{q}{V} = \frac{2\pi\epsilon_0}{\ln \frac{GMD}{r}} \text{ f/m}$$



20/5/4/6

$$C = \frac{2\pi\epsilon_0}{\ln \frac{GMD}{r}} \quad (F/m)$$

$$C = 0.055 \quad (\mu F/km)$$

$$\ln \frac{GMD}{r}$$

for bundle conduction

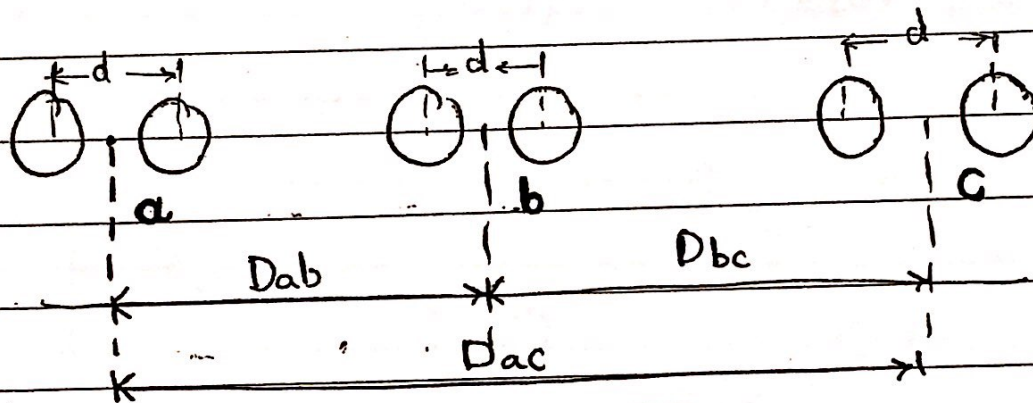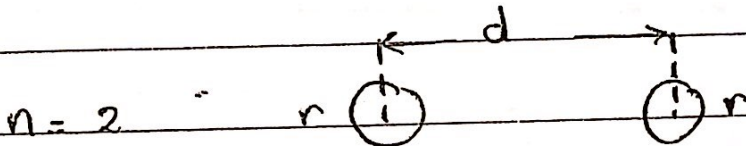


$r(b) = \text{bundle}$

$$C = \frac{2\pi\epsilon_0}{\ln \frac{GMD}{r(b)}}$$

$$r(b) = \sqrt{r d}$$

$n=3$

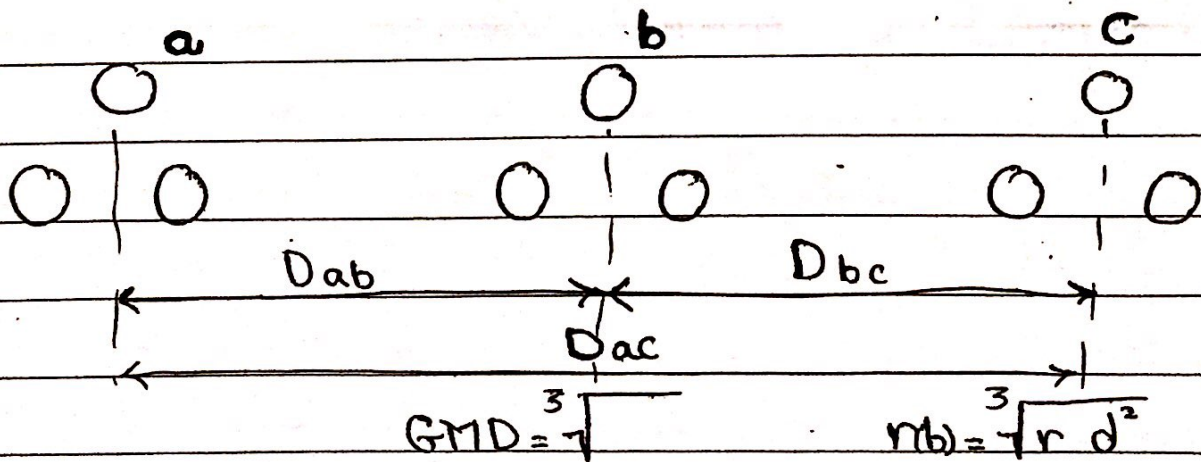


$$GMD = \sqrt[3]{\dots}$$

$$r(b) = \sqrt[3]{r d^2}$$

(8)


$$n = 4$$

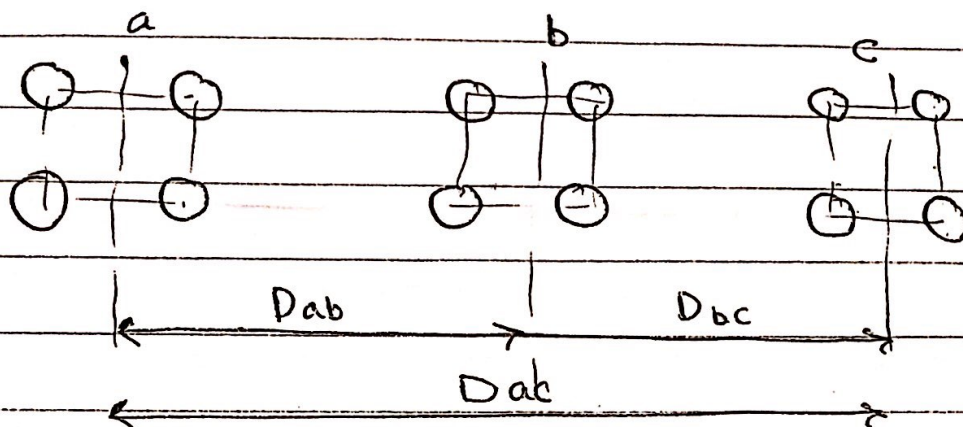


$$r(b) = \sqrt[4]{r d^3} \cdot (1.09)$$

* Ex :- # 1

$$d = 18 \text{ in}$$

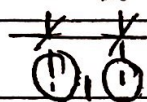

35 ft

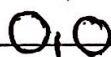

35 ft



$$\text{diam} = 0.977 \text{ inch}$$


Solution

$$GMD = \sqrt[3]{(35)(35)(35)} = 44.087 \text{ ft}$$

$$r(b) = \frac{\sqrt{(0.977)^2 \times 18}}{12} = 0.12471 \text{ ft}$$

$$C = \frac{0.0556}{\ln \frac{44.087}{0.12471}} = 0.0107 \text{ } \mu\text{F/km}$$

* Ex :- # 2

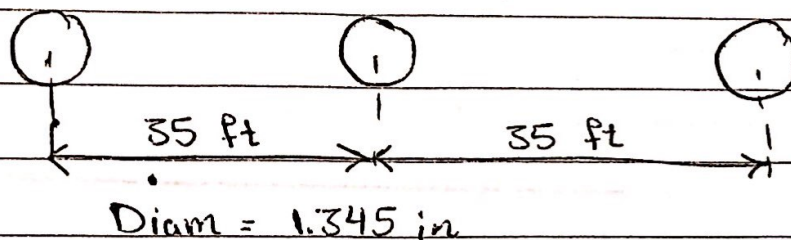Solution


$$r = (1.345 / 2) / 12 = 0.056 \text{ ft}$$

$$C = \frac{0.0556}{\ln \frac{44.097}{6.056}} = 0.0083 \text{ } \mu\text{F/km}$$

$$\% \text{ increase in } C = \frac{0.0107 - 0.0083}{0.0083} \times 100$$

$$\approx 28.9\%$$

Capcitanace for duble Circuit line :-

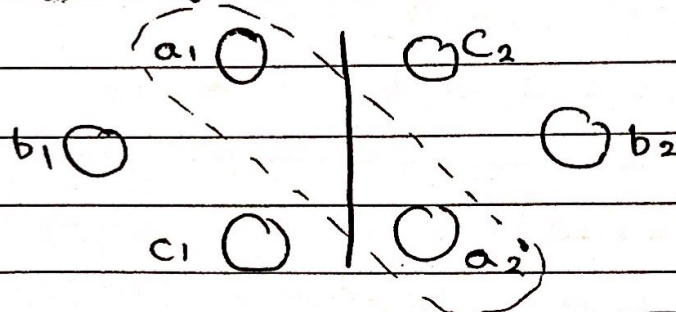

$$C = \frac{2\pi \epsilon_0}{\ln \frac{GMD}{GMR_c}}$$

GMD :- Same as inductance

for GMR_c ?


$$r_A = \sqrt{r D_{a_1 a_2}}$$

$$r_B = \sqrt{r D_{b_1 b_2}}$$

$$r_C = \sqrt{r D_{c_1 c_2}}$$

$$GMR_c = \sqrt[3]{r_A r_B r_C}$$

Ex :- # 3

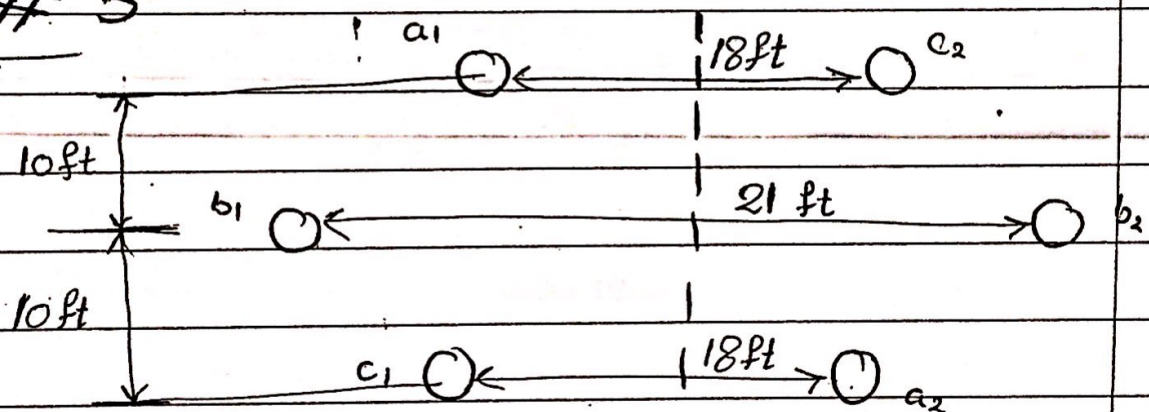

solution

Tables

$$\text{Diam} = 0.68 \text{ in}$$

$$r = \frac{0.68}{2 \times 12} = 0.0283 \text{ ft}$$

$$GMD = 16.1 \text{ ft}$$

$$D_{a_1 a_2} = D_{c_1 c_2} = \sqrt{18^2 + 20^2} = 26.9 \text{ ft}$$

$$D_{b_1 b_2} = 21 \text{ ft}$$

$$r_A = r_C = \sqrt{0.0283 \times 26.9} = 0.873 \text{ ft}$$

$$r_B = \sqrt{0.0283 \times 21} = 0.7709 \text{ ft}$$

$$GMR_C = \sqrt[3]{(0.873)^2 \times 0.7709} = 0.837 \text{ ft}$$

$$C = \frac{0.0556}{\ln \frac{16.1}{0.837}} = 18.807 \times 10^{-12} \text{ F/m} = 0.018807 \text{ } \mu\text{F/km}$$

* Capacitive Susceptance?

$$B_C = \frac{1}{X_C}$$

$$B_C = 2\pi f C$$

$$= 2\pi (60) (18.807 \times 10^{-12}) \text{ S} \cdot \frac{1609 \text{ m}}{\text{mi}} \cdot \frac{1}{\text{mil}}$$

$$= 11.41 \times 10^{-6} \text{ S/mil/phase}$$

#2

2015/4/6

Use of tables :-

$$X_L = 2\pi f L$$

$$X_L = 2\pi f (2 \times 10^{-7} \ln \frac{GMD}{GMR})$$

$$= 4\pi f \times 10^{-7} \ln \frac{D_m \rightarrow \text{mutual}}{D_s \rightarrow \text{self}} \quad (\Omega/\text{m})$$

$$= 4\pi f \times 10^{-7} \ln \frac{D_m}{D_s} \times \frac{\Omega}{\text{m}} \cdot \frac{1609\text{m}}{\text{mil}}$$

$$= 2.022 \times 10^{-3} f \ln \frac{D_m}{D_s} \quad (\Omega/\text{mil})$$

$$= 2.022 \times 10^{-3} f \ln \frac{1}{D_s} +$$

$$2.022 \times 10^{-3} f \ln D_m \quad (\Omega/\text{mil})$$

① inductive Reactance at 1-ft spacing :-


$$X_a = 2.022 \times 10^{-3} f \ln \frac{1}{D_s}$$

② inductive Reactance at spacing factor :-

$$X_d = 2.022 \times 10^{-3} f \ln D_m$$

Ex :- # 4

Partridge

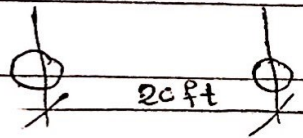

Single-ph line :-

find the inductive Reactance/mil ?

solution

$$GMR = D_s = 0.0217 \text{ ft}$$

$$X_L = 2\pi(60) \times 2 \times 10^{-7} \cdot \ln \frac{20}{0.0217} \times 1609 = 0.828 \text{ } \Omega/\text{mile}$$

using Table

$$X_a = 0.465 \text{ } \Omega/\text{mil}$$

$$X_d = 0.3635 \text{ } \Omega/\text{mil}$$

$$X_L = X_a + X_d$$

$$= 0.465 + 0.3635 = 0.8285 \text{ } \Omega/\text{mile}$$

$$X_{\text{line}} = 2 \times 0.8285 = 1.656 \text{ } \Omega/\text{mil}$$

$$X_d = 0.2794 \log d$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi f (2\pi \epsilon_0)}$$

$$X_C = \frac{2.862 \times 10^9}{f} \ln\left(\frac{D}{r}\right) \quad \Omega\text{-m}$$

$$X_C = \frac{2.862 \times 10^9}{f} \ln\left(\frac{D}{r}\right) \times \frac{1 \text{ mil}}{1609 \text{ m}}$$

$$X_C = \frac{1.779 \times 10^6}{f} \ln\left(\frac{D}{r}\right) \quad (\Omega\text{-mil to neutral})$$

$$X_C = \frac{1.779}{f} \times 10^6 \ln \frac{1}{r} + \frac{1.779 \times 10^6}{f} \ln D$$

Capacitive Reactance to neutral at 1-ft spacing :-

$$X_d = \frac{1.779 \times 10^6}{f} \ln \frac{1}{r}$$

Capacitive Reactance spacing factor :-

$$X_d' = \frac{1.779 \times 10^6}{f} \ln D$$

* Ex :- 5 # :-

$$X_d' = 0.1074 \text{ M}\Omega\text{-mil}$$

$$X_d' = 0.0889 \text{ M}\Omega\text{-mil}$$

$$X_C = X_d' + X_d' = 0.1963 \text{ M}\Omega\text{-mil/cond}$$

$$X_{C_{\text{line to line}}} = 2 \times 0.1963 \times 10^6 = 0.392 \text{ M}\Omega\text{-mil}$$


$$B_c = \frac{1}{X_C} = 2.55 \times 10^{-6} \text{ S/mil}$$

* to Calculate Charging Current :-

(a) single-Phase Lines :-

$$I_{\text{charge}} = B_{L-L} \cdot V_{L-L}$$

$$= j\omega C_{a-b} \cdot V_{a-b}$$

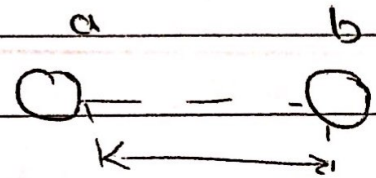

(b) 3-Ph Line :-

$$I_{\text{charge}} = V_{ph} \cdot B_{\text{to neutral}}$$

$$= j\omega C_n \cdot V_{an}$$

Quiz #1 : solution :-

AAC (61) strand , 1113000 CMil

$$R_{dc}(20^{\circ}) = 0.01552 \times 10^{-3} \Omega/\text{ft}$$

$$R_{ac}(60\text{Hz}, 50^{\circ}) = 0.0951 \Omega/\text{mil}$$

1.6% spiraling

a)

$$R_{20} = \rho \frac{L}{A}$$

$$= \frac{17 \Omega\text{-CMil}}{\cancel{\text{ft}}} \times \frac{1 \cancel{\text{ft}}}{1113000 \cancel{\text{CMil}}} \times 1.016 = 1.552 \times 10^{-5} \Omega/\text{ft}$$

b)

$$\frac{R_{ac}}{R_{dc}}$$

$$R_{dc}(50^{\circ}) = R_{dc}(20) \frac{50 + T}{20 + T} = \frac{1.552 \Omega}{\cancel{\text{ft}}} \times \frac{5280 \cancel{\text{ft}}}{\text{mil}}$$

$$R_{dc}(50^{\circ}) = 0.01552 \times 10^{-3} \left(\frac{228.1 + 50}{228.1 + 20} \right) \times 5280$$

$$= 0.0918 \Omega/\text{mil}$$

$$\% \text{ increase in } (R) = \frac{0.0951 - 0.0918}{0.0918} \times 100 = 3.5\%$$

* Ex :- #1 :-


(Drake)
ACSR

find the Cap (C),

Cap Reactance (X_c), $f = 60\text{Hz}$

Line length is 17.5 mil and at (220 kV)

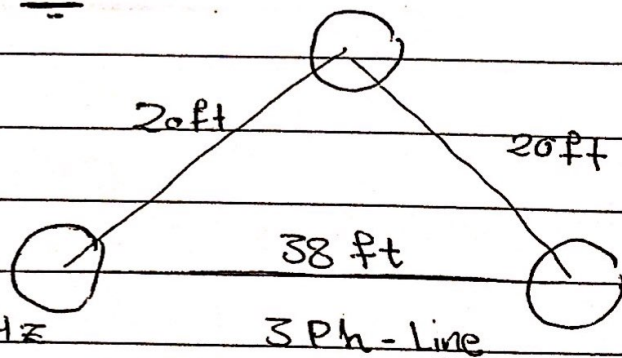find the total Cap. Reactance or to neutral and Charge Current.



$$C = \frac{2\pi\epsilon_0}{\ln \frac{D_{eq}}{r}} \quad (F/m)$$

$$D_{eq} = \sqrt[3]{26 \times 20 \times 38} = 24.8 \text{ ft}$$

$$r = \frac{1.108}{2 \times 12} = 0.0462 \text{ ft}$$

$$C = \frac{2\pi \times 8.8 \times 10^{-12}}{\ln \frac{24.8}{0.0462}} = 8.8 \times 10^{-12} \text{ F/m}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi(60) \times 8.8 \times 10^{-12} \text{ F/m}} = \frac{1}{1609 \text{ m}\Omega/\text{mil}} = 1 \Omega\text{-m}$$

$$= 0.1865 \times 10^6 \Omega\text{-mil to neutral} = 0.1865 \text{ M-mil-}\Omega$$


$$(X_C) \text{ for the line} = \frac{0.1865 \text{ M-}\Omega\text{-mil}}{175 \text{ mil}} = 1066 \Omega\text{-to neutral}$$

$$I_{ch} = W C_n V_{ph} = 2\pi(60) (8.8 \times 10^{-12} \text{ F/m} \times \frac{1609 \text{ m}\Omega/\text{mil}}{\text{mile}}) \times 175 \text{ mil} \times \frac{(220 \times 10^3)}{\sqrt{3}} = 119 \text{ A} = 0.68 \text{ A/mil}$$

$$I_{ch} = \frac{(220 \times 10^3 / \sqrt{3}) \text{ V}}{1066 \Omega} = \frac{V}{X_C}$$

$$I_{ch} = 1$$


* effect of Earth on the Capacitance:

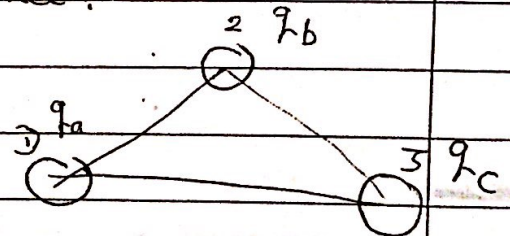

$$C_n = 2\pi \epsilon_0$$

$$\ln \frac{D}{r} - \ln \left(\frac{\sqrt[3]{H_{12} H_{13} H_{23}}}{\sqrt[3]{H_1 H_2 H_3}} \right)$$

3-Ph
Voltage Lin-Lin
 $\sqrt{3} * V$

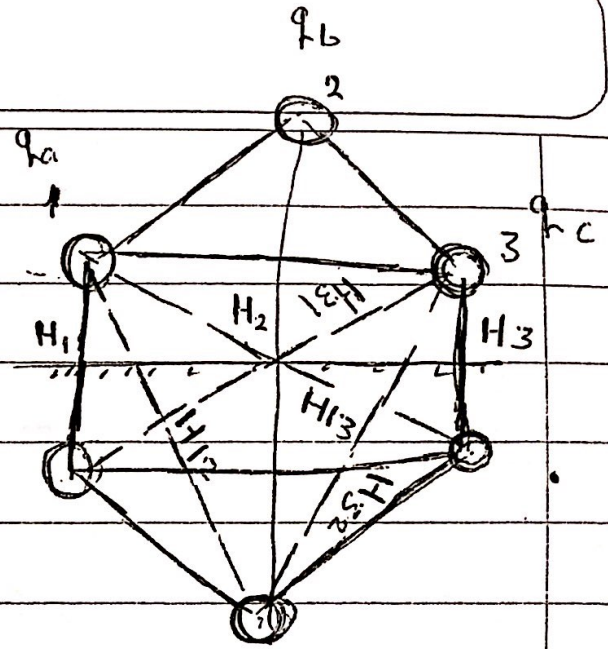


2015/4/9

Transmission line model :-


* Line performance under normal operating conditions :-

 $(V_{LN}, I) \rightarrow (\text{Per Phase})$

$$V_{LN} = \frac{1}{\sqrt{3}} V_{ph}$$

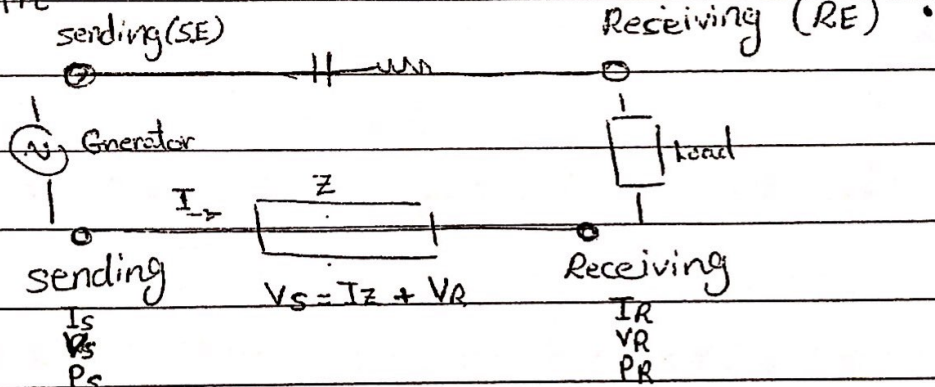* (R, L, C) * (R, XL, XC) ① short line $l \leq 80 \text{ km} = 50 \text{ mil}$

(C) is neglected

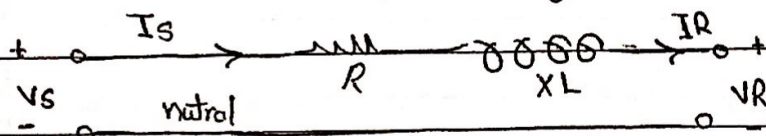

$$Z = R + jXL$$

$$V_s = V_R + I_R Z \rightarrow \textcircled{1}$$


$$I_s = I_R$$

$$I_s = I_R \rightarrow \textcircled{2}$$

$$Z = (r + j\omega L) * l$$

length

$$r = \Omega/\text{km} \quad l = \text{H}/\text{km}$$

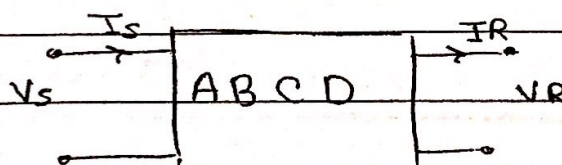 $Z \equiv \text{total line impedance } (\Omega)$ 

from ①①' and ②②'

$$A = 1$$

$$B = Z$$

$$C = 0$$


$$D = 1 = A$$

$$V_s = A V_R + B I_R \rightarrow \textcircled{1'}$$

$$I_s = C V_R + D I_R \rightarrow \textcircled{2'}$$

Voltage regulation (VR) :-

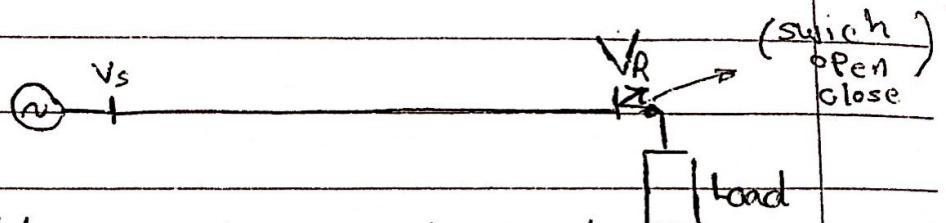
الفرق في الجهد في حالة وجود Load وعدم وجود Load
Receiving



The Voltage Regulation is the percentage change in Voltage at the (R.E) in the line (expressed as percent of F.L Voltage) in going from load to full load.

$$\% VR = \frac{|V_R (\text{no-load})| - |V_R (\text{Full-load})|}{|V_R (\text{Full-load})|} \times 100 = \%$$

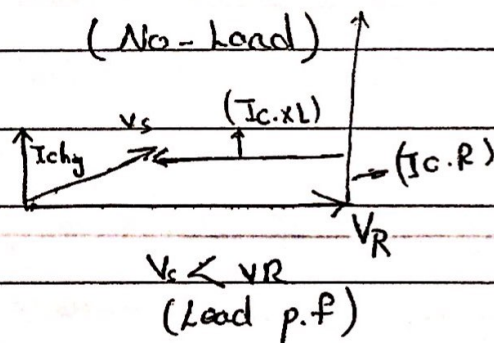Ferranti-effect
حيث ظاهرة الجهد في نهاية الخط في حالة No load




$$L \rightarrow (I \rightarrow \text{يتأخر } 90^\circ \rightarrow V)$$

$$C \rightarrow (I \rightarrow \text{يسبق } 90^\circ \rightarrow V)$$

$$R \rightarrow (I = V \angle 0^\circ)$$

(Load)

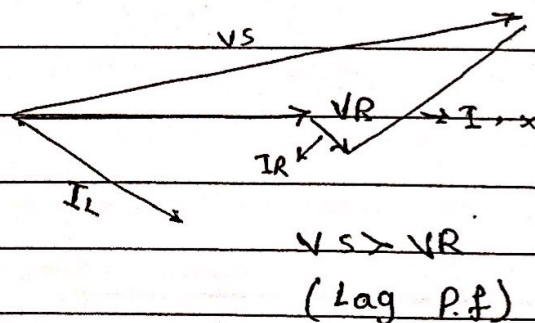

2015 / 4 / 13

$$\text{efficiency of line } (\eta) = \frac{P_R(3\phi)}{P_S(3\phi)}$$

$$\eta = \frac{80}{90}$$

Ex: # 1

A 220 kV, 3-Ph, 60 Hz Transmission line is 40 km long.

$$r = 0.15 \Omega / \text{Ph} / \text{km}$$

$$L = 1.3263 \text{ mH} / \text{ph} / \text{km}$$

C = neglected

The load at (R.E) is (381 MVA) at (0.8 P.F) lag and 220 kV. Using short line model find the voltage And power at the (S.E) and (VR) and (η)

solution

$$S = 381 \text{ MVA}$$

IR

$$I_R = \frac{381 \times 10^3 \text{ KVA}}{\sqrt{3} \times 220 \text{ kV}} \angle -\cos^{-1} 0.8 = 1000 \angle -36.87^\circ \text{ A}$$




$$Z = [0.15 + j(2\pi \times 60 \times 1.3263 \times 10^{-3})] \times 40 \text{ km}$$

$$Z = 6 + j20 \Omega$$

$$V_S = V_R + I_R \cdot Z$$

$$= \frac{220}{\sqrt{3}} \angle 0^\circ + [(1000 \angle -36.87^\circ) + j(6 + j20)] \times 10^{-3}$$
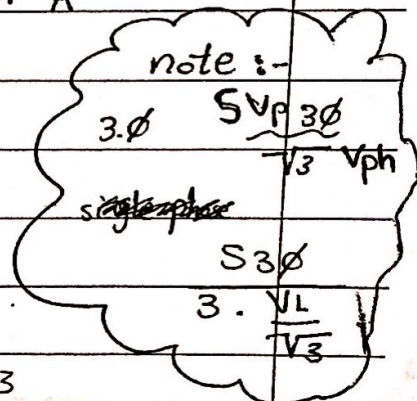
$$V_S = 1.44.33 \angle 4.93^\circ \text{ kV (phase)}$$



VR

36.87

$$V_s(L-L) = \sqrt{3} \times 144.33$$

$$= 250 \text{ kV}$$

$$S_s = V_s I_s^*$$

$$S_{s(3ph)} = 3 (144.33 \angle 4.93^\circ) (1000 \angle +36.87^\circ)$$

$$= 432.990 \angle 41.80^\circ$$

$$P_s = 432.99 \cos 41.8^\circ = 322.78 \text{ MW}$$

$$P_R = 304.8 \text{ MW}$$


$$\eta = \frac{P_R}{P_s} \times 100 = \frac{304.8}{322.78} \times 100 = 94\%$$

$$\text{Voltage Regulation} = \frac{|V_s| - |V_R|}{|V_R|} \times 100$$

$$= \frac{250 - 220}{220} \times 100 = 13.6\%$$


* medium-length line model

$$80 \text{ km} < L < 250 \text{ km}$$

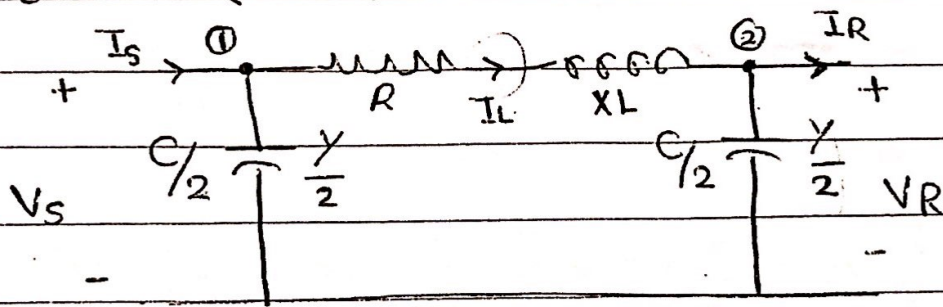

nominal- π model

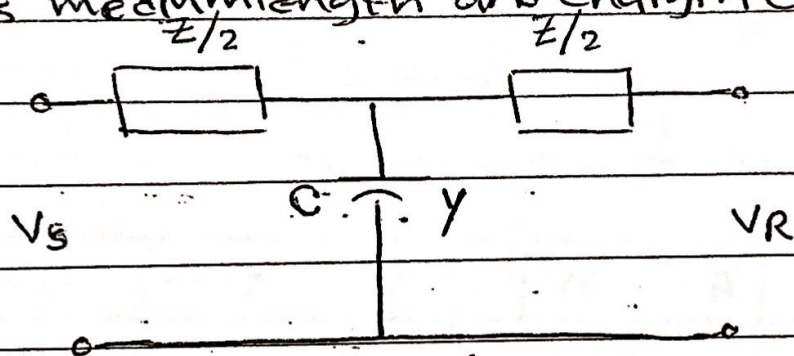The line is medium length and charging current increases



the capacitance must be taken into account

$$Y = G + j\omega C$$

$$G = \frac{1}{Z_0}$$

$$Y = j\omega C$$

$$Y/2 = \frac{\omega C}{2}$$

at node 2 KCL:

$$I_1 = I_R + \frac{Y}{2} \cdot V_R \quad \text{--- (1)}$$

KVL:

$$V_S = V_R + I_1 Z \quad \text{--- (2)}$$

$$V_S = V_R + Z \left[I_R + \frac{Y}{2} V_R \right]$$

$$V_S = V_R + Z I_R + \frac{ZY}{2} V_R$$

$$V_S = V_R \left(1 + \frac{ZY}{2} \right) + Z I_R$$

$$V_S = A V_R + B I_R$$

$$A = 1 + \frac{ZY}{2}$$

$$B = Z$$

$$C = Y \left(1 + \frac{ZY}{4} \right)$$

$$D = A = \left(1 + \frac{ZY}{2} \right)$$

node ① KCL :-

$$I_s = I_L + V_s \frac{Y}{2}$$

$$I_s = I_R + \frac{Y}{2} V_R + \frac{Y}{2} \left[\left(1 + \frac{ZY}{2}\right) V_R + Z I_R \right]$$

$$I_s = I_R + \frac{Y}{2} V_R + \frac{Y}{2} V_R + \frac{Y}{2} \cdot \frac{ZY}{2} V_R + \frac{YZ}{2} I_R$$

$$I_s = Y \left(1 + \frac{ZY}{4}\right) V_R + \left(1 + \frac{ZY}{2}\right) I_R$$

$$I_s = C V_R + D I_R$$

$$\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$$

$$AD - BC = 1$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix} \Rightarrow \begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix}^{-1} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

$$V_R = D \cdot V_s - B \cdot I_s$$

$$I_R = -C V_s + A \cdot I_s$$

* Ex :- #2 ^{Design Voltage} A 345-kv, 3-Ph transmission line is 130 km long.

$$r = 0.036 \, \Omega/\text{Ph}/\text{km}$$

$$L = 0.8 \, \text{mH}/\text{Ph}/\text{km}$$

$$C = 0.0112 \, \mu\text{F}/\text{km}$$

H.W #1

the load at the R.E is 270 MVA at 0.8 p.f lag
at 325 kv. using medium model

find V_s , P_s , V_R ?

Line \leftarrow \rightarrow (3-ph)

 V_s

R.E

$$V_R = \frac{325}{\sqrt{3}} \angle 0^\circ$$

- 270 MVA
- 0.8 lag
- 325 kv

$$I_R = I_L = \frac{270 \times 10^3 \text{ kVA}}{\sqrt{3} \times 325} \angle -36.87^\circ = 479.64 \angle -36.87^\circ$$

$$A = 1 + \frac{ZY}{2}$$

$$Z = (0.636 + j(2\pi \times 60 \times 0.8 \times 10^{-3})) \times 130$$

$$A = D$$

$$Y = j\omega C = j(2\pi \times 60 \times 0.0112 \times 10^{-6}) \times 130$$

$$C = Y(1 + \frac{ZY}{4})$$

$$D = A$$

$$V_R = \frac{|V_{R \text{ No. Load}}| - |V_{R \text{ Full-Load}}|}{|V_{R \text{ Full-Load}}|}$$

$$= \frac{(V_s/A) - V_R}{V_R}$$

$$V_s = 199.187 \angle 4.012 \text{ kv/ph}$$

$$I_s = 421.127 \angle -25.56^\circ \text{ A}$$


$$S_s = 251.64 \text{ MVA} \angle 29.572^\circ$$

$$P_s = 218.868 \text{ MW}$$

$$P_R = 215.99 \text{ MW}$$

2015/4/16

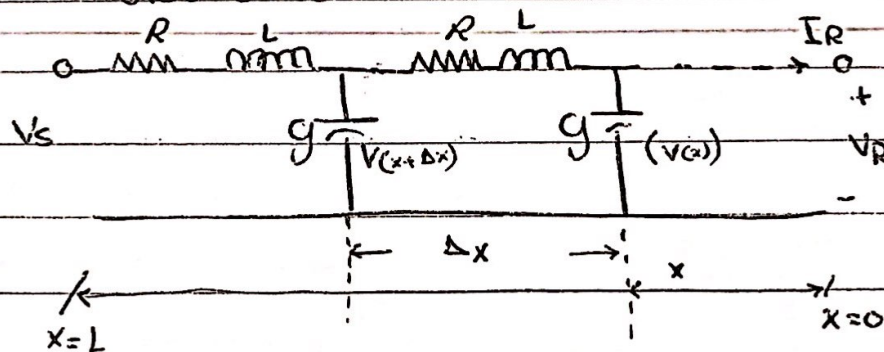* Long-line model $\Rightarrow L > 250 \text{ km}$
 the parameters (r, l, c) are uniformly distributed.



$$Z = r + j\omega l / \text{unit length} = Z \Delta x$$

$$y = \cancel{r} + j\omega c / \text{unit length} = y \Delta x$$

For small segment of the line (Δx) at a distance (x) from (R.E)

* KVL :-

$$V(x + \Delta x) = V(x) + Z \Delta x I(x)$$

$$\frac{V(x + \Delta x) - V(x)}{\Delta x} = Z I(x) \rightarrow (1)$$

take limit as $\Delta x \rightarrow 0$

$$\frac{dV(x)}{dx} = -Z I(x) \rightarrow (2)$$

* KCL :-

$$I(x + \Delta x) = I(x) + y \Delta x V(x + \Delta x)$$

$$\frac{I(x + \Delta x) - I(x)}{\Delta x} = y V(x + \Delta x)$$

take limit as $\Delta x \rightarrow \infty$

$$\frac{dI(x)}{dx} = y V(x) \rightarrow (3)$$

$$\text{diff (2)} \Rightarrow \frac{d^2 V(x)}{dx^2} = -Z \frac{dI(x)}{dx} \rightarrow (4)$$

$$\frac{d^2 V(x)}{dx^2} = -Z y V(x) \Rightarrow \boxed{ZY = \gamma^2} \quad \#$$

$$\boxed{\frac{d^2 V(x)}{dx^2} = \gamma^2 V(x)}$$

solving this (2nd) order diff eqn :

$$V(x) = A_1 e^{\gamma x} + A_2 e^{-\gamma x} \rightarrow (5)$$

$\gamma = \sqrt{YZ}$: is known as the propagation Constant, a Complex

$$\gamma = \alpha + j\beta$$

α = Attenuation Constant nepers/(km) or (mil)

β = Phase Constant rad/(km) or (mil)

$$(1) \rightarrow I(x) = \frac{1}{Z} \frac{dV(x)}{dx}$$

$$= \frac{\gamma}{Z} [A_1 e^{\gamma x} - A_2 e^{-\gamma x}]$$

$$= \sqrt{\frac{Y}{Z}} [A_1 e^{\gamma x} - A_2 e^{-\gamma x}]$$

$$= \frac{1}{\sqrt{ZY}} (A_1 e^{\gamma x} - A_2 e^{-\gamma x})$$

Let $Z_c = \sqrt{Z/Y}$ = characteristic impedance

$$I(x) = \frac{1}{Z_c} (A_1 e^{\gamma x} - A_2 e^{-\gamma x})$$

$$\begin{array}{cc} | & | \\ x=L & x=0 \\ V_S & V_R \end{array}$$

at $(x=0)$, $V(0) = V_R$

$$V_R = A_1 + A_2$$

$$I_R = \frac{A_1 - A_2}{Z_c}$$

$$A_1 = (V_R + Z_c I_R)/2 , A_2 = (V_R - Z_c I_R)/2$$

$$V(x) = \frac{V_R + Z_c I_R}{2} e^{\gamma x} + \frac{V_R - Z_c I_R}{2} e^{-\gamma x}$$

$$I(x) = \frac{(V_R/Z_c + I_R)}{2} e^{\gamma x} - \frac{(V_R/Z_c - I_R)}{2} e^{-\gamma x}$$

* re-arranging

$$V(x) = \frac{e^{\gamma x} + e^{-\gamma x}}{2} V_R + Z_c \frac{e^{\gamma x} - e^{-\gamma x}}{2} I_R$$

$$\begin{aligned} V(x) &= \cosh(\gamma x) V_R + Z_c \sinh(\gamma x) I_R \\ &= A V_R + B I_R \end{aligned}$$

$$A = \cosh(\gamma x)$$

$$B = Z_c \sinh(\gamma x)$$

$$I(x) = \frac{1}{Z_c} \frac{e^{\gamma x} - e^{-\gamma x}}{2} V_R + \frac{e^{\gamma x} + e^{-\gamma x}}{2} I_R$$

$$= \frac{1}{Z_c} \sinh(\gamma x) V_R + \cosh(\gamma x) I_R$$

$$\begin{cases} C = 1/Z_c \sinh(\gamma x) \\ D = A = \cosh(\gamma x) \end{cases}$$

$$V(L) = V_{\text{Send}}$$


$$I(L) = I_{\text{Send}}$$

$$\begin{pmatrix} V_{S(x)} \\ I_{S(x)} \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} V_R \\ I_R \end{pmatrix}$$

$$V(0) = V_{\text{Rec}}$$

$$I(0) = I_R$$

Equivalent - (PI model)

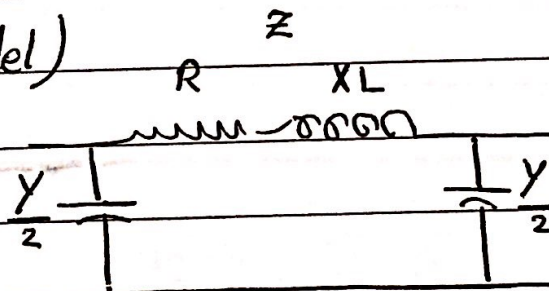

nominal (PI)

$$V_S = \left(1 + \frac{ZY}{2}\right) V_R + Z I_R$$

$$I_S = \left(1 + \frac{ZY}{4}\right) Y V_R + \left(1 + \frac{ZY}{2}\right) I_R$$

①

$$V_S = \left(1 + \frac{Z'Y'}{2}\right) V_R + Z' I_R$$

$$I_S = \left(1 + \frac{Z'Y'}{4}\right) Y' V_R + \left(1 + \frac{Z'Y'}{2}\right) I_R$$

Equivalent (PI model)

$$\textcircled{2} \quad V_s = \cosh(\gamma L) V_R + Z_c \sinh(\gamma L) I_R$$
$$I_s = \frac{1}{Z_c} \sinh(\gamma L) V_R + \cosh(\gamma L) I_R$$

Comparing (1), (2)

$$Z' = Z_c \sinh(\gamma L) = Z_c \frac{\sinh(\gamma L)}{\gamma L}$$

$$\frac{Y'}{2} = \frac{1}{Z_c} \tanh\left(\frac{\gamma L}{2}\right) = \frac{Y}{2} \frac{\tanh(\gamma L/2)}{(\gamma L/2)}$$


(H.W #2)

2015/4/20


Ex :- #1 long line

A single-circuit, (60 Hz), (3-ph) transmission line is (230 mil) long, The conductors are (Rook) with a flat horizontal spacing of (23.8 ft).

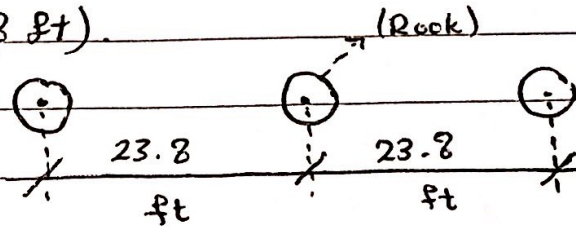the load on the line is (125 MW) at (215 kV),
Unity (P.F).



Find the Voltage, Current and
Power at the (S.E) and
voltage Regulation.

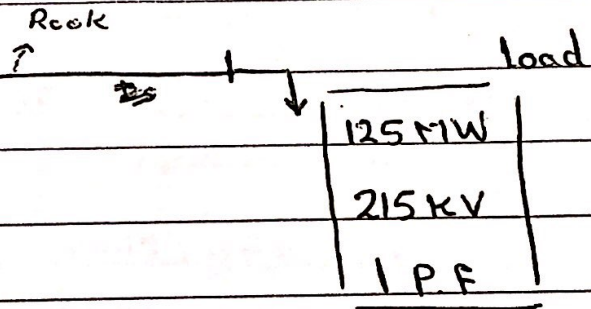solution

$$V_s = A V_R + B I_R$$

$$A = \cosh(\gamma L)$$

$$B = Z_c \sinh(\gamma L)$$

$$V_R = \frac{215}{\sqrt{3}} \angle 0^\circ \text{ V}, \quad I_R = \frac{125 \times 10^3}{\sqrt{3} \times 215 \times 1} \angle 0^\circ \text{ A}$$

$$\gamma = \sqrt{ZY}$$

$$Z = r + jX_L$$

use Table at (50°C) Rook

$$r = 0.1603 \text{ } \Omega/\text{m}$$

$$X_L = X_a + X_d$$

$$\text{for } X_a = 0.415 \text{ } \Omega/\text{mil}$$

$$\text{for } X_d \Rightarrow GMD = \sqrt[3]{(23.8)(23.8)(47.6)} \\ = 30 \text{ ft}$$

$$X_d = 0.4127 \text{ } \Omega/\text{mil}$$

$$X_L = X_a + X_d = 0.8277 \text{ } \Omega/\text{mil}$$

$$* Z = 0.1603 + j0.8277 \Omega/\text{mil}$$

$$y = j\omega c = j \frac{1}{x_c}$$

use Table

$$x_c = x_a' + x_d'$$

$$\text{for } x_a' = 0.095 \text{ M}\Omega\text{-mil}$$

$$\text{for } x_d' = 0.1009 \text{ M}\Omega\text{-mil}$$

$$x_c = 0.1959 \times 10^6 \Omega/\text{mil}$$

$$* y = j \frac{1 \times 10^{-6}}{0.1959} \text{ S/mi} = 5.105 \times 10^{-6} \angle 90^\circ \text{ S/mil}$$

$$Z = 0.8431 \angle 79.04^\circ \Omega/\text{mil}$$

$$y = 5.105 \times 10^{-6} \angle 90^\circ \text{ S/mil}$$

$$x = \alpha + j\beta = \sqrt{Zy} = \sqrt{(0.8431) \times (5.105 \times 10^{-6})} \angle \frac{90 + 79.04}{2}$$

$$\gamma L = 230 \times \sqrt{Zy} = 0.4772 \angle 84.52^\circ$$

$$A = \cosh \gamma L = \cosh(\alpha L) \cdot \cos(\beta L) + j \sinh(\alpha L) \cdot \sin(\beta L)$$

$$B = jZ_c \sinh(\gamma L)$$

$$Z_c = \sqrt{Z/y} = \sqrt{\frac{0.8431}{5.105 \times 10^{-6}}} \angle \frac{79.04 - 90}{2} \rightarrow \text{Range } (0 \rightarrow -15^\circ)$$

$$Z_c = 406.4 \angle -5.48^\circ \Omega$$

$$V_{\text{lin}} = \sqrt{3} V_{\text{ph}}$$

$$V_s = A V_R + B I_R = V_{s(\text{ph})}$$

$$I_s = C V_R + D I_R$$

$$C = j \frac{1}{Z_c} \sinh(\gamma L)$$

$$D = A$$

$$P_s = 3 V_{s(\text{ph})} \cdot I_s \cos \theta_s$$

$$S_{s(3\phi)} = 3 \bar{V}_{s(\text{ph})} \bar{I}_s^* = 11 \angle \theta$$

(NOTE BOOK)

$$\text{Voltage Regulation} = \frac{|V_S/A| - |V_R|}{|V_R|} \times 100 =$$

* Lossless Line :-

$$\gamma = \alpha + j\beta = \sqrt{(r + j\omega L)(G + j\omega C)}$$

$$= j\omega \sqrt{LC}$$

$\alpha = 0$ no Attenuation

$$j\beta = j\omega \sqrt{LC} \quad \beta = \omega \sqrt{LC}$$


$$Z_C = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{r + j\omega L}{G + j\omega C}}$$

$$Z_C = \sqrt{\frac{L}{C}} \equiv \text{Surge impedance}$$

* SIL :-

surge impedance loading

$$Z = \frac{|V|^2}{S^*}$$

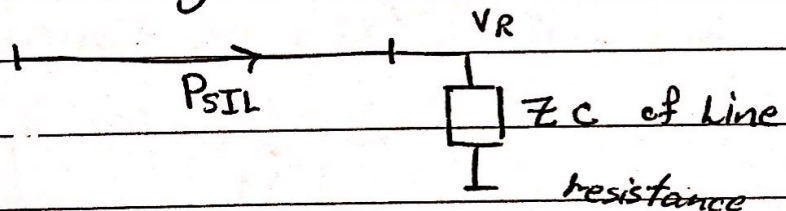

$$I_R = \frac{V_R}{\sqrt{\frac{L}{C}}} = \frac{V_R}{Z_C}$$

$$P = 3V_{\phi} I$$

$$P = 3 \frac{V_L}{\sqrt{3}} \times \frac{V_L}{\sqrt{3}} \times \frac{1}{\sqrt{L/C}}$$

$$P = \frac{|V_L|^2}{Z_C} \text{ (MW)}$$

* SIL :- Surge impedance loading of a line is the power delivered by the line to a purely

Resistive load equal to its surge impedance.

* Wave length (λ) :-

is the distance along a line between two points of a wave which diff 2π or 360°

$$\lambda = \frac{2\pi}{\beta} \text{ (km) or (mil)}$$

* Velocity of propagation of wave :- (km/s)

$$V = \lambda \text{ (km)} \times f \text{ (Hz)} \quad \text{(mil/s)}$$

$$V = \frac{2\pi}{\beta} \times f$$

$$\lambda = 5000 \text{ km}$$

$$V = 3 \times 10^8 \text{ m/s} //$$

$$V = \frac{1}{\sqrt{LC}}$$

$$V_s = \cosh(\gamma L) V_R + \sinh(\gamma L) Z_c I_R$$

$$\cosh(\gamma L) = \cosh(\alpha L) \cdot \cos(\beta L) + j \sinh(\alpha L) \underbrace{\sin(\beta L)}_{\text{Zero}}$$

$$\cosh(\gamma L) = \cos(\beta L)$$

$$\sinh(\gamma L) = j \sin(\beta L)$$


$$V_s = \cos(\beta L) V_R + j Z_c \sin(\beta L) I_R$$

$$I_s = j \frac{1}{Z_c} \sin(\beta L) V_R + \cos(\beta L) I_R$$

For lossless

2015/4/30

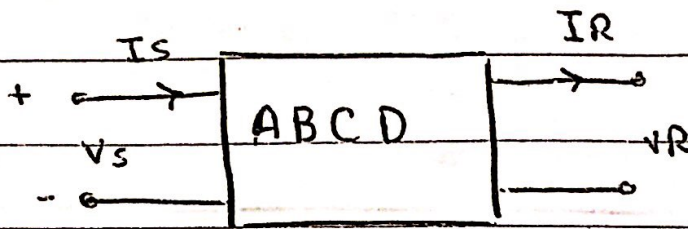* Complex power flow through a transmission line is



$$V_s = A V_R + B I_R$$

$$I_s = C V_R + D I_R$$

$$(Power Angle) \quad S = P_{R(3\phi)} + j Q_{P(3\phi)} \quad (Receiver \ 3\phi)$$

$$\text{let } \bar{V}_s = |V_s| \angle \delta, \quad \bar{V}_R = |V_R| \angle 0^\circ$$

$$\bar{A} = |A| \angle \theta_A, \quad \bar{B} = |B| \angle \theta_B$$

$$I_R = \frac{V_s - A V_R}{B} = \frac{|V_s| \angle \delta - |A| \angle \theta_A |V_R| \angle 0^\circ}{|B| \angle \theta_B}$$

$$= \frac{|V_s|}{|B|} \angle \delta - \theta_B - \frac{|A| |V_R|}{|B|} \angle \theta_A - \theta_B$$

Power flow
منروي هان يكون في
زاوية بين (R), (S)

$$S_{R(3\phi)} = 3 (V_R \cdot I_R^*)$$

Per Phase
وضعت في 3
باني تخطين
3 Phase

$$S_{R(3\phi)} = 3 |V_R| \angle 0^\circ \left[\frac{|V_s|}{|B|} \angle \theta_B - \delta - \frac{|A| |V_R|}{|B|} \angle \theta_B - \theta_A \right]$$

$$S_{A(3\phi)} = 3 \frac{|V_s| |V_R|}{|B|} \angle \theta_B - \delta - 3 \frac{|A| V_R^2}{|B|} \angle \theta_B - \theta_A$$


* if (V_s) & (V_R) are line voltages:

$$= 3 \frac{V_s(L)}{\sqrt{3}} \frac{V_R(L)}{\sqrt{3}} \angle \theta_B - \delta - 3 A \left(\frac{V_R(L)}{\sqrt{3}} \right)^2 \angle \theta_B - \theta_A$$

$$S_{R(3\phi)} = \left| \frac{V_S(L)}{B} \frac{V_R(L)}{B} \right| / \theta_B^\circ - \delta^\circ - \left| \frac{A V_R(L)^2}{B} \right| / \theta_B^\circ - \theta_A^\circ$$

$$P_{R(3\phi)} = \left| \frac{V_S(L)}{B} \frac{V_R(L)}{B} \right| \cos(\theta_B^\circ - \delta^\circ) - \left| \frac{A V_R(L)^2}{B} \right| \cos(\theta_B^\circ - \theta_A^\circ)$$

$$Q_{R(3\phi)} = \left| \frac{V_S(L)}{B} \frac{V_R(L)}{B} \right| \sin(\theta_B^\circ - \delta^\circ) - \left| \frac{A V_R(L)^2}{B} \right| \sin(\theta_B^\circ - \theta_A^\circ)$$

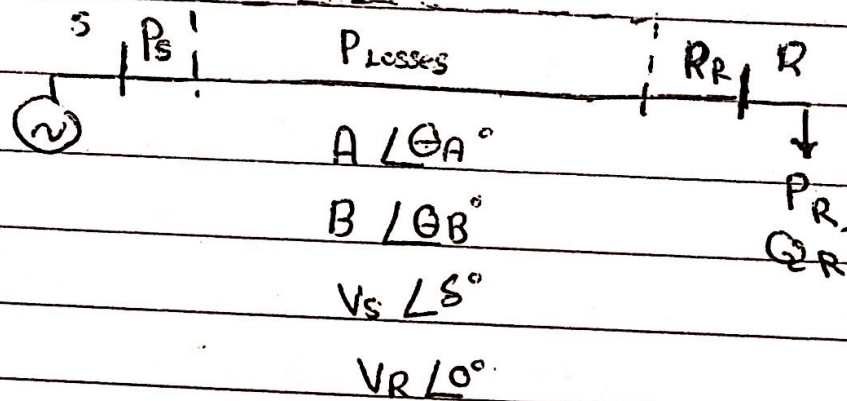

$$S_{S(3\phi)} = P_{S(3\phi)} + j Q_{S(3\phi)} = 3 V_S I_S^*$$

$$V_S = A V_R + B I_R \quad ; \quad I_S = C V_R + D I_R$$

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$\begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} * \frac{1}{|\Delta|} \begin{bmatrix} V_S \\ I_S \end{bmatrix}$$

$$* \quad |\Delta| = 1 \quad (AD) - (BC) = 1$$

$$(A = D)$$

$$V_R = A V_S - B I_S$$

$$I_S = \frac{A V_S - V_R}{B}$$

$$I_s = \left| \frac{A V_s}{B} \right| / \theta_A^\circ + \delta^\circ - \theta_B^\circ - \left| \frac{V_R}{B} \right| / -\theta_B^\circ$$

* Finally :-

$$P_s(3\phi) = \left| \frac{A V_s(L)^2}{B} \right| \cos(\theta_B^\circ - \theta_A^\circ) - \left| \frac{V_s(L) V_R(L)}{B} \right| \cos(\theta_B^\circ + \delta)$$

$$Q_s(3\phi) = \left| \frac{A V_s(L)^2}{B} \right| \sin(\theta_B^\circ - \theta_A^\circ) - \left| \frac{V_s(L) V_R(L)}{B} \right| \sin(\theta_B^\circ + \delta)$$

* Losses :-

Real and Reactive transmission line losses :-

$$P_{loss}(3\phi) = P_s(3\phi) - P_R(3\phi)$$

$$Q_{loss}(3\phi) = Q_s(3\phi) - Q_R(3\phi)$$


Capacitor
VAR is a
Generator

* Lossless line :-

$$B = Z = r + jx' \quad B = jx'$$

$$\theta_A = 0^\circ \quad \theta_B = 90^\circ$$

$$* P_R = \left| \frac{V_s V_R}{x'} \right| \sin \delta$$

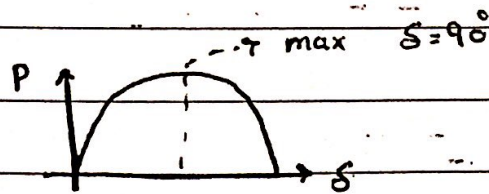

$$* Q_R = \left| \frac{V_s V_R}{x'} \right| \cos \delta - \left| \frac{V_R^2}{x'} \right| \cos \beta L$$

* Voltage \rightarrow (line-line)

2015/5/4

teterial #

A 69-kv, 3-Ph short transmission line is (16km) long, given :-

series impedance $Z = 0.125 + j0.4375 \Omega/\text{km/ph}$


The load at the (R.E) is :-

1) 70 MVA, (0.8 P.f) lag at (64 kv).

2) 120 MW, (1 P.f) lag at (64 kv).

Calculate the Voltage at (S.E), Power at (S.E) and (Voltage Regulation), (Efficiency).

Solution

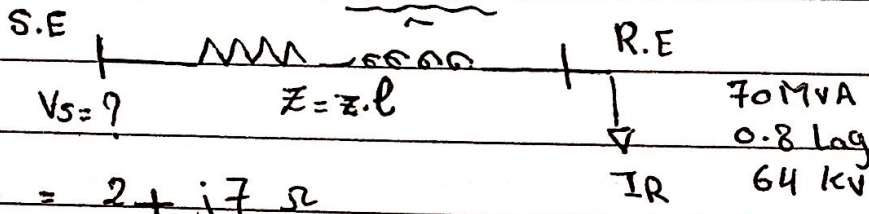

$$* Z = Z_l = 2 + j7 \Omega$$

$$* I_R = \frac{70 \times 10^3 \text{ KVA}}{\sqrt{3} \times 64 \text{ kV}} = \frac{1}{\sqrt{3}} \frac{1}{\cos^{-1} 0.8} = 631.48 \angle -36.87^\circ \text{ A}$$

$$V_s = A V_R + B I_R = (1) V_R + Z I_R = \frac{64 \times 10^3}{\sqrt{3}} \angle 0^\circ + Z (631.48 \angle -36.87^\circ)$$

$$V_s = 40.7 \angle 3.9^\circ \text{ kV / ph}$$

$$* \therefore V_s (\text{Line}) = \sqrt{3} \times 40.7 = 70.5 \text{ kV}$$

$$* P_s (3\phi) = 3 \cdot V_{sph} I_s \cos \theta_s$$

$$= 3 (40.7) (631.48) \cos (40.77)$$

$$= 58 \text{ MW}$$

$$* P_{loss} = 3 I^2 R = 3 (631.48)^2 \times 2$$

$$= 2.3 \text{ MW}$$


$$* S_g (3\phi) = 3 \bar{V}_{sph} I_s^* = 3 (40.7 \angle 3.9^\circ) (631.48 \angle 36.87^\circ)$$

$$= 77.1 \angle 40.77^\circ \text{ MW}$$

$$* V_{Regulation} = \frac{|V_s| - |V_R|}{|V_R|} \times 100 = \frac{70.5 - 64}{64} \times 100 = 10.2\%$$

NOTE BOOK
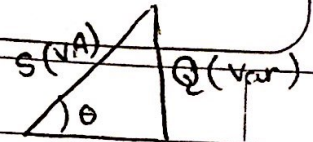
$$\eta = \frac{P_R}{P_S} \times 100 = 96.05\%$$




$$(B) \quad I_R = \frac{120 \times 10^3 \text{ kW}}{1 \times (\sqrt{3}) \times 64 \text{ kV}} \quad 10^\circ$$

$$P = S \cos \theta$$

$$Q = S \sin \theta$$

التي في

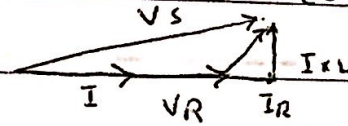

* Ex: 2 # A 230-kV, 3 Ph line has

$$Z = 0.05 + j0.46 \text{ } \Omega/\text{Ph/km}$$

$$Y = j3.4 \times 10^{-6} \text{ S/Ph/km} \quad b = 80 \text{ km}$$

using nominal- π model find:-

(a) ABCD Constant. (B) V_S, I_S, V_R, S_S, η

The load is 200 MVA at P.F 0.8, 220 kV


solution

$\rightarrow \log$

$$V_R = 220/\sqrt{3} \quad 10^\circ$$

$$Z = Z_L = 4 + j36 \text{ } \Omega$$

(A)

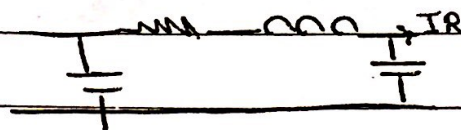

$$Y = jY_B$$

$$= j0.272 \times 10^{-3} \text{ S}$$

$$A = 1 + \frac{ZY}{2} = 0.9951 + j0.000544$$

$$B = Z = 4 + j36 \text{ } \Omega$$

$$C = Y(1 + \frac{ZY}{4}) = j0.0002713 \text{ S}$$

$$D = A$$

$$(B) \quad V_S = A V_R + B I_R = 140.1 \angle 5.7^\circ \text{ kV}$$

$$I_R = \frac{200 \times 10^3 \text{ kVA}}{\sqrt{3} \times 220 \text{ kV}} \quad 1 - \cos^{-1} 0.8$$

$$V_R = \frac{220 \text{ kV}}{\sqrt{3}}$$

$$I_R = 524.86 \angle -36.8^\circ \text{ A}$$

$$I_S = C V_R + D I_R = 502.4 \angle -33.6^\circ \text{ A}$$

$$S_S (3\text{Ph}) = 3 V_S I_S^* = 3 (140.1 \angle 5.7^\circ) (502.4 \angle 33.6^\circ)$$

$$= 211 \angle 39^\circ \text{ MVA}$$

$$V_{\text{Regulation}} = \frac{|V_S| - |V_R|}{|V_R|} \times 100 = 10.9\%$$

NOTE BOOK

67 | V R I

$$\eta = \frac{P_R}{P_S} \times 100 = \frac{200 \times 0.8}{211 \times \cos 39} \times 100 = 98\%$$

* For a lossless line: (2015/5/4)

$$r=0 \quad g=0$$

$$Z = \cancel{R}_{\text{Zero}} + jX_L = jX_L$$

$$Y = \cancel{G}_{\text{Zero}} + jB_C = jB_C$$

$$\theta_B = 90^\circ, \theta_A = 0^\circ$$

$$\gamma = \alpha + j\beta = \sqrt{ZY} = \sqrt{(jX_L)(jB_C)} = j\omega\sqrt{LC}$$

$$\alpha = 0 \quad \beta = \omega\sqrt{LC}$$

$$A = \cosh(\gamma l)$$

$$= \cosh \cancel{\alpha l}_{\text{Zero}} \cos \beta l + j \sinh \cancel{\alpha l}_{\text{Zero}} \sin \beta l$$

$$* A = \cos \beta l$$

$$B = Z_C \sinh \gamma l = Z_C [\sinh \cancel{\alpha l}_{\text{Zero}} \cos \beta l + j \cosh \cancel{\alpha l}_{\text{Zero}} \sin \beta l]$$

$$* B = jZ_C \sin \beta l$$

$$V_S = \cosh \gamma l V_R + Z_C \sinh \gamma l I_R \quad (\text{Lossy Line})$$

$$V_S = \cos \beta l V_R + j Z_C \sin \beta l I_R \quad (\text{Lossless Line})$$

2015/5/7


28/3/2017

AL: daerrey...

The distance between the conductors of a single-ph, 60-HZ line is 10 ft. Each conductor has 6 strands as shown. The diameter of each strand is 0.1 in. Find the inductance of the line in mH/mi and the line inductive reactance in ohms/Km.

Quiz #2

2015/4/16

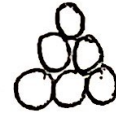

A 3-ph, 60-HZ line is 250 mi long. The parameters of the line are $R=0.2$ ohm/mi, $X=0.8$ ohm/mi, $Y=5.3 \times 10^{-6}$ S/mi.

- a- The S.E. voltage is 220KV, find the S.E. current when there is no load on the line.
- b- If the load at the R.E. is 80 MW at 220 KV with unity P.F., calculate the S.E. voltage

Quiz #3

A 3-ph 420-KV, 60-HZ transmission line is 460km long and can be assumed lossless. The line is energized with 420 KV at the S.E.

2015/6/18

Quiz #

When the load at the R.E. is removed, the voltage at the R.E. is 702 KV. Ideal reactors are to be installed at the R.E. to keep $|V_S| = |V_R| = 420$ KV when the load is removed. Determine the reactance per phase and the required 3-ph reactive power of the reactor.

- ① Principles of simulation design
- ② modeling Method
- ③ Performance Evaluation and Result Analysis.
- ④ Programming in Matlab.
- ⑤ Matlab comm sys tools.
- ⑥ simulation Applications. (mini project)

$$S = 3 V_{(PL)} I_s^*$$

$$S = 3 (V_{3\phi}) I_s$$


$$S = \cancel{3} \left(\frac{V_L}{\cancel{\sqrt{3}}} \right) I_s$$

$$S = \sqrt{3} V_L I_s$$

$$I_s = \frac{S}{\sqrt{3} V_L}$$

9/2015/5/11

Loadability Curves

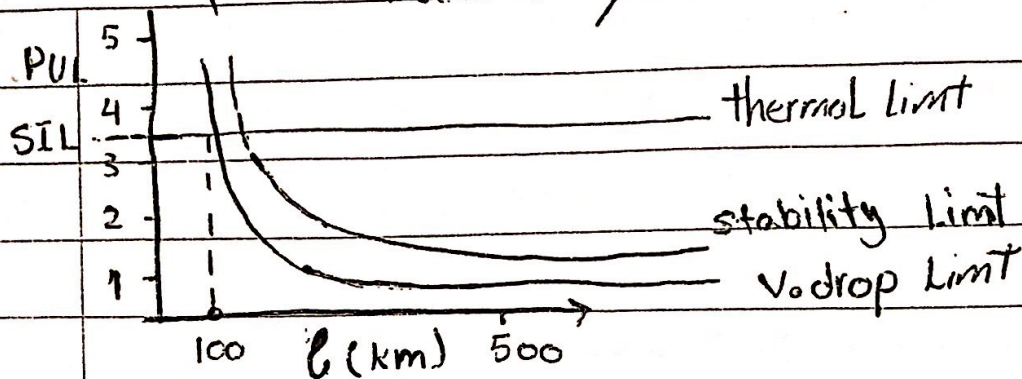


$$P = 3.5 \times SIL \quad SIL = \frac{V^2}{Z_c}$$

$$= 1400 \text{ MWatt}$$

$l (400 \text{ km})$


$$P = 1.25 \times SIL$$

$$= 1.2 \times 400 = 480 \text{ MWatt}$$

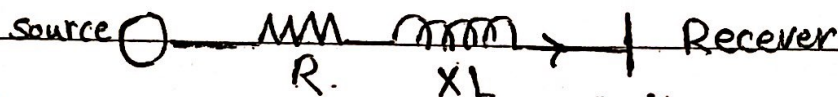


$$V_{\text{drop}} = I^2 Z \quad , \quad \frac{V_R}{V_S} \geq 0.95$$

$$V_R = 0.95 V_S$$

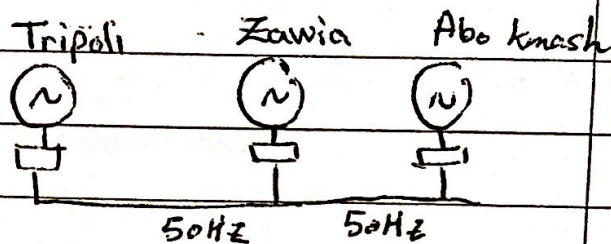

(synchronous
generations)



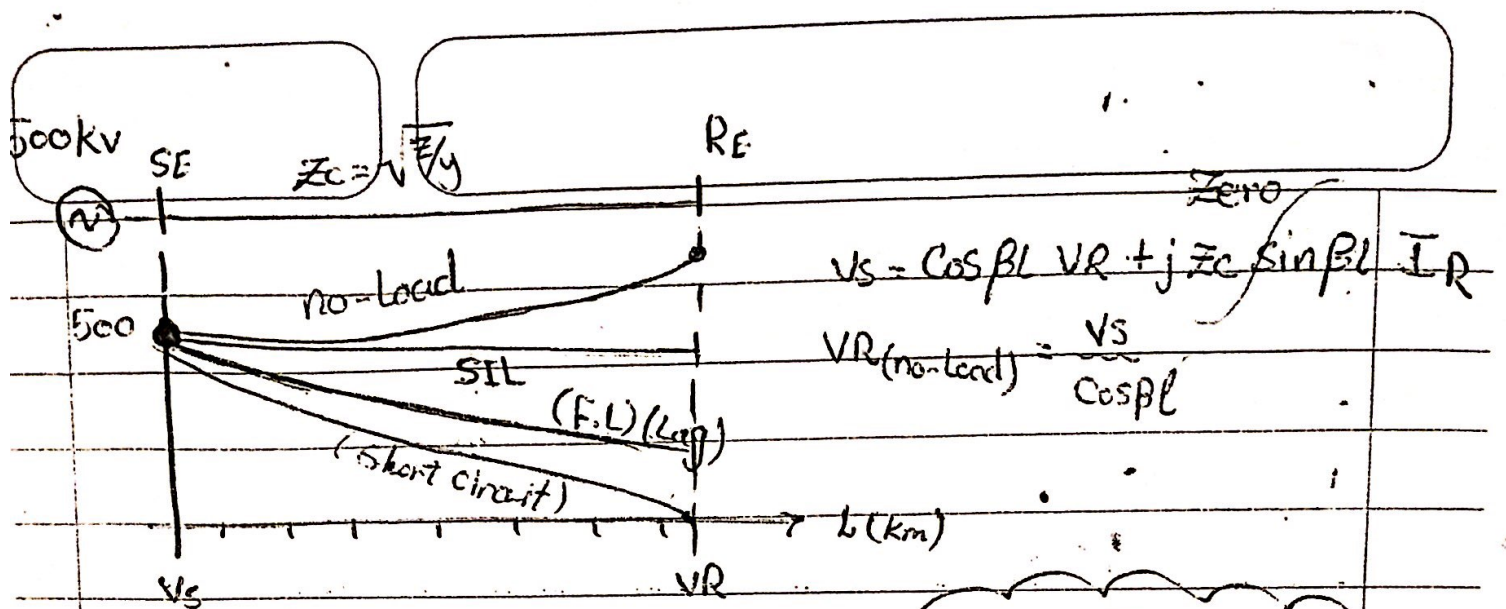

$$V_S = \cos \beta l V_R + j Z_c \sin \beta l I_R$$

$$V_R(\text{no-load}) = \frac{V_S}{\cos \beta l}$$

* Ferranti - effect :-

الارتفاع في الجهد الطرفي لأعلى من الجهد

(no-load) بيزاري بسبب

(charging current)

SIL :-

Power - Real

$Z_c = R$ Power loss

* under (SIL) the voltage magnitude ~~angle~~ along this line is constant and equals (V_R).

$$V_S = V_R (\cos \beta l + j \sin \beta l)$$

$$V_S = |V_R| \angle \theta_R = \beta l$$

* Ex :- (1) A 3-ph, 765 kV, 60 Hz, 300 km transmission line it has

$$Z = 0.0165 + j0.3306 \Omega/\text{km/ph}$$

$$Y = j4.674 \times 10^{-6} \text{ S/km/ph}$$

- 1) Find the exact ABCD constants.
- 2) Compare the exact (B) with that of the nominal (π) circuit. and ($1/2$)
- 3) Assuming the lossless line find the theoretical steady-state stability limit for the line assuming $\lambda = 5000 \text{ km}$, $V_S = V_R = 765 \text{ kV}$
- 4) calculate the (P_{\max}) (Practical) which can be transmitted given $\delta = 35^\circ$

(NOTE BOOK)

Solution

$$Z_c = \sqrt{Z/Y} = 266.1 \angle -1.43^\circ$$

$$A = \cosh(\gamma L) = D$$

$$\gamma L = \sqrt{ZY} \cdot l = 0.3731 + j0.37$$

$$B = Z_c \sinh(\gamma L)$$

$$= 0.3731 \angle 88.57^\circ$$

$$C = 1/Z_c \sinh(\gamma L)$$

$$A = D = \cosh(0.3731 \angle 88.57^\circ) = 0.9313 \angle 0.209^\circ \text{ per unit}$$

$$B = Z_c \sinh(\gamma L) = 97.1 \angle 87.2^\circ \Omega \rightarrow (\text{exact}) \#$$

$$C = 1/Z_c \sinh(\gamma L) = 1.37 \times 10^{-3} \angle 90.06^\circ \text{ S}$$

$$B_{(\text{nominal})} = Z \cdot l = 99.3 \angle 87.2^\circ \Omega \rightarrow (\text{nominal}) \#$$

$$\frac{|B_{\text{exact}} - B_{\text{nominal}}|}{|B_{\text{nominal}}|} \times 100 = \frac{99.3 - 97.1}{97.1} \times 100 = 2.3\%$$

$$(Y/2) = \frac{Y}{2} \cdot l = 7.011 \times 10^{-4} \angle 90^\circ \text{ S (nominal)}$$

$$(Y/2) = \frac{\cosh(\gamma L) - 1}{Z_c} = 7.095 \times 10^{-4} \angle 89.97^\circ \text{ S (exact)}$$

$$(Y/2) \approx (Y/2) \approx 1\%$$

For lossless line

$$P = \frac{V_s \cdot V_R}{X} \sin \delta = \left(V_s (\text{pu}) \cdot V_R (\text{pu}) \cdot \frac{SIL}{\sin(\frac{2\pi}{\lambda} l)} \right) \sin \delta$$

$$(V_s/V_{\text{rated}}) = 1 = (765/765) = 1 \text{ per unit}$$

$$(V_R/V_{\text{rated}}) = 1 \text{ per unit}$$


$$(SIL) = \frac{(V_{\text{rated}})^2}{Z_c} = (765)^2 / (266.1) = 2199 \text{ MWatt}$$

$$(study \text{ step}) P = (1)(1)(2199) \sin(90^\circ) = 5974 \text{ MWatt}$$

$$P = SIL \times 2.72$$

$$(SIL) \times 2.72$$

$$= (2199)(2.72) = 5974 \text{ MWatt}$$

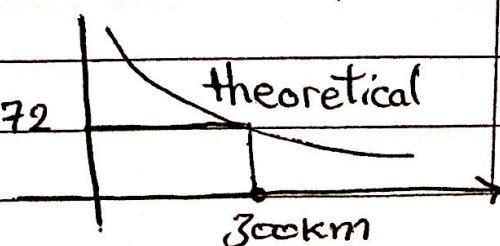

NOTE BOOK

$$P = \frac{V_s \cdot V_R}{B} \cos(\theta_B - \delta) - \frac{A V_R^2}{B} \cos(\theta_B - \theta_A)$$


$$P = \frac{(765)(765)}{97.1} \cos(87.2 - 35) - \frac{0.9313 (765)^2}{97.1} \cos(87.2 - 0.209)$$

$$P \approx 3300 \text{ MWatt} \rightarrow \text{practical power}$$

section of transmission line

2015/5/14

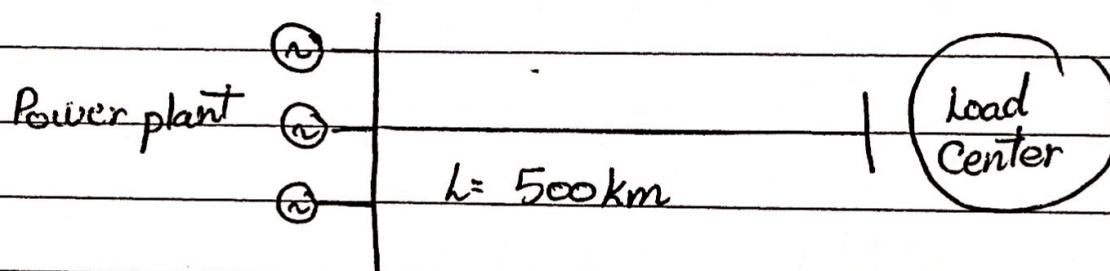Voltage and number of lines for Power transfer so



* Ex:- From a power plant, (9000 MW) are to be transmitted to a load Center located (500 km) from the power plant. Based on practical line loadability Criterion, determine the number of (3-ph) (60 Hz) lines required to transmit this power with One line Out of service, for the following cases :-

- 345-kv , $Z_C = 297 \Omega$
- 500-kv , $Z_C = 277 \Omega$
- 765-kv , $Z_C = 266 \Omega$

solution

neglecting line losses :-

$$P = \frac{V_S V_R \sin \delta}{x'} = \frac{V_S(\text{pu}) \cdot V_R(\text{pu}) (\text{SIL}) \sin \delta}{\sin(2\pi l/\lambda)}$$

Assume $V_S = 1 \text{ pu}$ $V_R = 0.95 \text{ pu}$
 $\delta = 35^\circ$ $\lambda = 5000 \text{ km}$

a) 345 kv $P/\text{line} = \frac{(1)(0.95)(401 \text{ MW}) \sin(35^\circ)}{\sin(2\pi \frac{500}{5000})} = 372 \text{ MW}$
 $\text{SIL} = \frac{(345)^2}{(297)} = 401 \text{ MW}$
 $\therefore \text{no of 345 kv lines} = \frac{9000}{372} + 1 \approx 26$

b) 500 kv $\text{SIL} = \frac{(500)^2}{277} = 903 \text{ MW}$ $P/\text{line} = \frac{(1)(0.95)(903 \text{ MW}) \sin 35^\circ}{\sin(2\pi \frac{500}{5000})}$
 $P/\text{line} = 837 \text{ MW}$
 $\therefore \text{no of line} = \frac{9000}{837} + 1 \approx 12$

c) 765 kv $\text{SIL} = \frac{(765)^2}{266} = 2200 \text{ MW}$ $P/\text{line} = \frac{(1)(0.95)(2200) \sin 35^\circ}{\sin(2\pi \frac{500}{5000})}$
 $P/\text{line} = 2039 \text{ MW}$ $\text{no of line} = \frac{9000}{2039} + 1 \approx 6$


increasing the ~~load~~ level from 345 kv to 765 kv has decreased the no of (3ph) line from (26 \rightarrow 6)

final

* Transmission line Compensation

- * at (SIL) :- the voltage along the line is constant
- * at (no-load & light-load) :- condition (V_R) is high \rightarrow shunt reactor is needed.

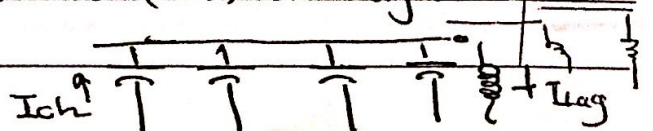في حالة الحمل الخفيف
 الجهد يكون مرتفعاً
 فنحتاج إلى مفاعل متوازي




V_S

long line

less less line

 V_R I_R

$$I_R = \frac{V_R}{X_{Lsh}} \quad (1)$$

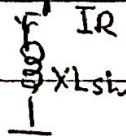

$$V_S = \cos(\beta l) V_R + j Z_c \sin(\beta l) I_R \quad (2)$$

① into ② for I_R

$$V_S = \cos(\beta l) V_R + j Z_c \sin(\beta l) \cdot \frac{V_R}{j X_{Lsh}}$$

$$V_S = \left(\cos(\beta l) + Z_c \sin(\beta l) / X_{Lsh} \right) V_R$$

$$X_{Lsh} = \frac{\sin(\beta l)}{\frac{V_S}{V_R} - \cos(\beta l)} Z_c$$

$$\text{for } V_S = V_R, \quad X_{Lsh} = \left(\frac{\sin(\beta l)}{1 - \cos(\beta l)} \right) Z_c$$

$$Z = \frac{|V|^2_{\text{rated}}}{S^*}$$

$$S = \frac{|V_{\text{rated}}|^2}{Z^*}$$


$$Q = \frac{|V_{\text{rated}}|^2}{X_L}$$

$$\text{①/phase} \rightarrow V_{L-N}$$

$$\text{②/line} \rightarrow V_{L-L}$$

* note:- At (SIL)

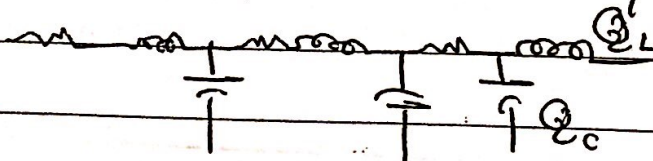
② generated by shunt cap = ② absorbed by series reactor



2015/5/18

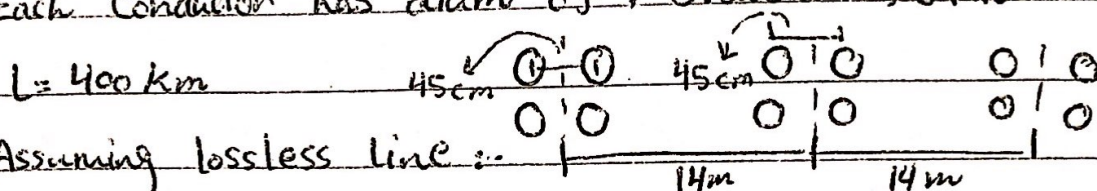* Problem (5-8) sadat :-

A (3-Ph), 765 kV, 60-Hz line has four ACSR 1431000 cmil 45/7 Bobolink conductor/Ph and flat horizontal spacing of (14m). Each Conductor has diam of, 3.625 cm, GMR = 1.439 cm



Assuming lossless line :-

a) Find the (char impedance), phase constant, wave length, SIL, ABCD Constant.

b) Find the (R.E) quantities when (1920 MW) and (600 MVAR) are transmitted at (765 kV) at (S.E) -

Solution

a) $Z_c = \sqrt{L/C}$

$L = 0.2 \ln \frac{GMD}{GMR} \text{ (mH/km)}, \quad GMD = \sqrt[3]{14 \times 14 \times 28} = 17.6 \text{ m}$

$GMR^b = 1.09 \sqrt[4]{1.439 \times (45)^3} = 20.74 \text{ cm}$

$L = 0.2 \ln \left(\frac{17.6}{0.2074} \right) = 0.89 \text{ mH/km}$

$C = 0.0556 / \ln \left(\frac{GMD}{r^b} \right)$

$r^b = 1.09 \sqrt[4]{\left(\frac{3.625}{2} \right)^3 \times 45^3} = 21.97 \text{ cm}$

$C = 0.0566 / \ln \left(\frac{17.6}{0.2197} \right) = 12.68 \times 10^{-3} \text{ F/km}$

* $Z_c = \sqrt{L/C} = 265 \Omega$

* $\beta = \omega \sqrt{LC} = 1.26 \times 10^{-3} \text{ rad/km}$


* $\lambda = 2\pi/\beta = 4986 \approx 5000 \text{ km}$

* $SIL = \frac{V_{rated}^2}{Z_c} = \frac{(765)^2}{265} = 2208 \text{ MW}$

* $A = \cos(\beta L) = 0.876$

* $B = j12.8 \quad \# \quad C = j1/Z_c \sin \beta L = 1.822 \times 10^{-3}$

* $D = A = 0.876$

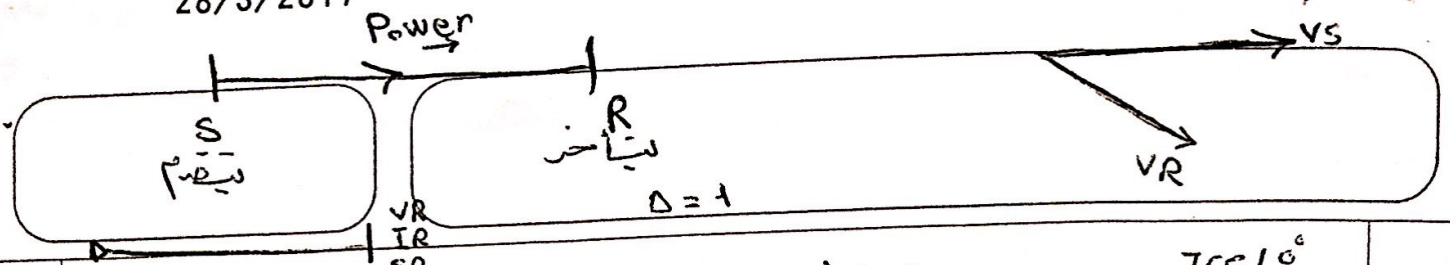

$$\begin{pmatrix} V_s \\ I_s \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_R \\ I_R \end{pmatrix} \Rightarrow \begin{pmatrix} V_R \\ I_R \end{pmatrix} = \begin{pmatrix} D & -B \\ -C & A \end{pmatrix} \begin{pmatrix} V_s \\ I_s \end{pmatrix}$$

$$V_s = \frac{765 \angle 0^\circ}{\sqrt{3}}$$

$$I_s = \frac{S^*}{\sqrt{3} V_s^*} = 1518.14 \angle -17.4^\circ \text{ A}$$

$$441672.95$$

$$V_R = 0.87 \angle 0^\circ \left(\frac{765 \times 10^3 \angle 0^\circ}{\sqrt{3}} \right) - 1281.9^\circ (1518.14 \angle -17.4^\circ)$$

$$V_R = 375 \text{ kv} \angle -29.6^\circ$$

$$V_R(L-L) = 649.5 \text{ kv} \angle -29.6^\circ$$

$$I_R = -C V_s + D I_s$$

(H.W) #3

$$I_R = 1325.28 \angle -161.989^\circ \text{ A}$$

- c) if the line is terminated in a pure resistive load, find the (S.E) quantities & voltage regulation when the (R.E) load resist is 264.5 Ω at 735 kv

2015 / 5 / 21

* Ex :- (2)

A (3-ph) line 300 mil long serves a load of 400 MVA 0.8 PF lag at 345 kv. The (ABCD) constants of the line are $(A=D=0.818 \angle 11.3^\circ)$, $(B=172.2 \angle 84.2^\circ \Omega)$, $(C=0.001933 \angle 90.45^\circ)$

- a) find the no-load voltage at the (R.E), voltage regulation.

- b) A 250-MVAR, 345 kv shunt reactor with $Y = -j0.0021$ is connected at the (R.E) at no-load, ① find the Equivalent (ABCD) for the line & reactor.

- ② repeat (a) using the equiv (ABCD).

Solution

$$V_S = A V_R + B I_R$$

$$V_R(\text{no-load}) = \frac{V_S}{A}$$

$$V_R = \frac{345}{\sqrt{3}} \angle 0^\circ \text{ kV}$$

$$I_R = \frac{400 \times 10^3 \angle -36.87^\circ}{\sqrt{3} \times 345} = 669.41 \angle -36.87^\circ \text{ A}$$

$$V_S = A V_R + I_R B = 256 \angle 20^\circ$$

$$V_S(\text{L}) = \sqrt{3} \times 256 = 443.75$$

$$V_R(\text{no-load}) = \frac{V_S}{A} = 542$$

$$\therefore \text{Regulation} = \frac{542 - 345}{345} \times 100 = 57\%$$

$$b) \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{eqw}} = \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{line}} \times \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{reactor}}$$

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} 1 & 0 \\ 0.0021j & 1 \end{pmatrix} = \begin{pmatrix} 1.177 \angle -0.8^\circ & 172.2 \angle 84.2^\circ \\ 2.17 \times 10^4 \angle 83.2^\circ & 0.818 \angle 1.3^\circ \end{pmatrix}$$

$$V_R(\text{no-load}) = \frac{256}{1.17} = 217.31 \text{ (phas)}$$

$$= 376.4 \text{ (line)}$$

$$\therefore \text{Regulation} = \frac{376.4 - 345}{345} \times 100 = 9.1\%$$


* series Capacitor Compensation

$$\uparrow P = \frac{V_s V_R}{X - jX_{c \text{ series}}} \sin \delta$$

$$Q_L = |I|^2 X_L$$

$$jX_{c \text{ series}}$$

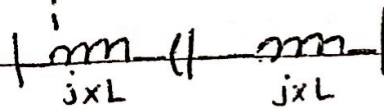* The series Cap is used to raise the line power capacity.



* (V) drop is decreased \rightarrow (V) regulation

$$Q_C = |I|^2 X_C$$

* line stability is improved

reactive power is

Varied Can Currently.

$$\frac{X_{c \text{ series}}}{X} = \text{percent compensation (25} \rightarrow \text{75\%)} \quad * \text{ Capacitor = VAR Generation}$$

* Ex :- (1) :-

A (3-ph) line, 60 Hz, 500 kV, 300 km, has

$$L = 0.97 \text{ mH/Ph/km}, \quad C = 0.0115 \text{ } \mu\text{F/Ph/km}$$

Assume a lossless line :-

* The Load at the (R.E) is (1000 MVA), 0.8 P.f lag at 500 kV.

a) find (Vs) & V (regulation)

b) series Cap are installed at the (mid-point) of the line providing (40%) comp & find (Vs) & V (regulation).

Solution

$$a) \quad V_R = \frac{500 \angle 0^\circ}{\sqrt{3}} = 288 \text{ kV}$$

$$I_R = \frac{1000 \times 10^3}{\sqrt{3} \times 500} \angle -36.87^\circ = 1154 \angle -36.87^\circ \text{ A}$$

$$L = 0.97 \text{ mH/Ph/km}$$

$$C = 0.0115 \text{ } \mu\text{F/Ph/km}$$

$$\beta = \omega \sqrt{LC} \ell = 2\pi(60) \sqrt{(0.97 \times 10^{-3})(0.0115 \times 10^{-6})} \times 300 \times \frac{180}{\pi} = 21.64^\circ$$

$$Z_C = \sqrt{\frac{L}{C}} = 290.48$$

$$V_S = (\cos 21.64)(288) + j 290 = 356.5 \angle 16.11^\circ \text{ kV}$$

$$\text{Voltage Regulation} = \frac{|V_S| - V_R}{V_R} \times 100 \approx 23\%$$

NOTE BOOK

$$X_{Cseries} = 0.4 \times 107.11 = 42.8$$

$$X = X' - X_{Cseries} = 107.11 - 42.8$$

$$Z' = 64.62 = B_{new}$$

$$A = 1 + \frac{Z' Y'}{2}$$



$$Y' = j0.0013165$$

$$A_{new} = 1 + \frac{Z' Y'}{2}$$

$$V_S = A_{new} V_R + B_{new} I_R = 326.4$$


$$\text{Regulation \%} = \frac{|V_S/A| - V_R}{V_R} \times 100 = 9.5 \%$$

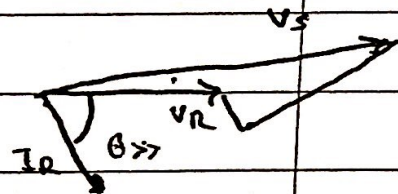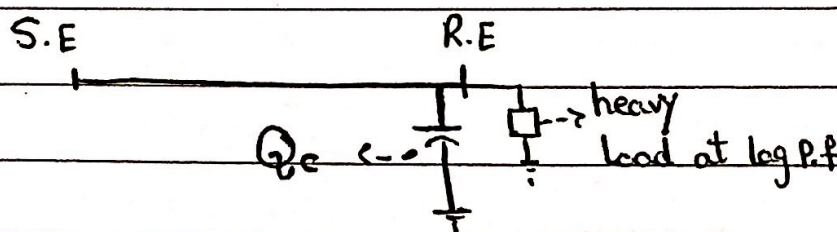* Shunt - Capacitor Compensation → 2015/5/28



* Lossless line

$$Q_R = \frac{|V_S V_R|}{X'} \cos \delta - \frac{V_R^2}{X'} \cos \phi_l$$

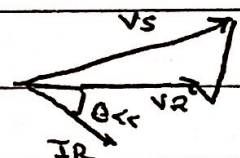

* ~~Example~~

shunt (cap) are used for lagging P.f circuits Created by heavy loads These (cap) supply the Required reactive power to maintain the (R.E) voltage at a Certain level.

* Ex :- (1)


A 3φ line 60 Hz, 500 kV, 300 km has

$$L = 0.97 \text{ mH/ph/km}, \quad C = 0.0115 \text{ μF/ph/km}$$

line is lossless, the load at R.E is (1000 MW) (0.8)

(NOTE BOOK)

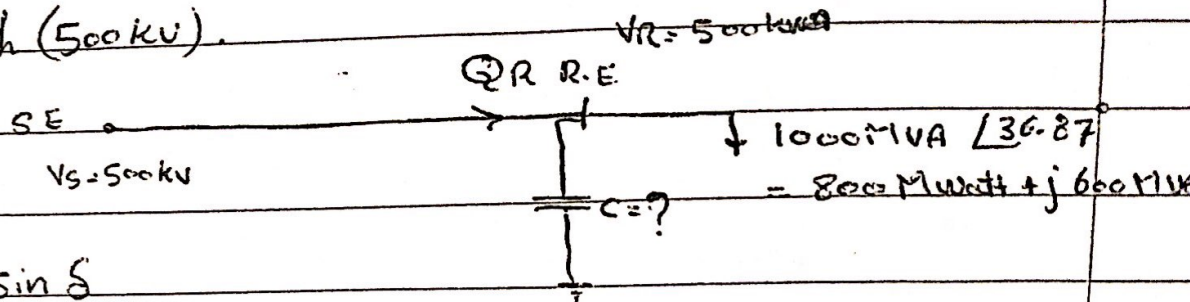2. 500kV, Determine the (MVAR) & (Cap) of the shunt (caps) to be installed at the (R.E) to keep (VA) at 500kV when the line is energized with (500kV).



$$P_{3\phi} = \left(\frac{V_s V_R}{x'} \right) \sin \delta$$

$$x' = Z_c \sin \beta l = 107.11 \Omega$$


$$Z_c = \sqrt{\frac{L}{C}} = 290.43 \Omega$$

$$\beta l = \omega \sqrt{LC} l = 21.64^\circ$$

$$800 = \frac{500 \times 500}{107.11} \sin \delta \Rightarrow \delta = 20.044^\circ$$

$$Q_{R3\phi} = \frac{V_s V_R \cos \delta}{x'} - \frac{V_R^2}{x'} \cos \beta l = \left(\frac{500^2}{107.1} \right) \cos(20.044) - \left(\frac{500^2}{107.1} \right) \cos 21.64^\circ$$

$$Q_{R3\phi} = 23.15 \text{ MVAR}$$

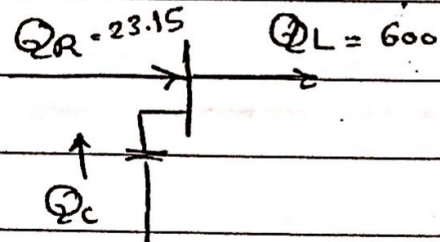



$$Q_R + Q_C = Q_L$$

$$Q_C = 600 - 23.15 = j 576.85 \text{ MVAR}$$

$$X_C = \frac{|V|^2}{S_C} = \frac{500^2}{j 576.85} = -j 433.38 \Omega$$

$$X_C = \frac{1}{\omega C}$$
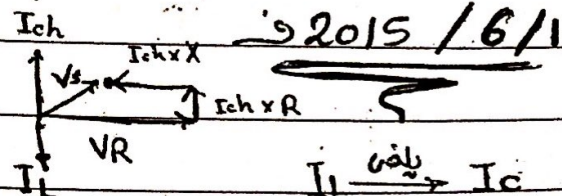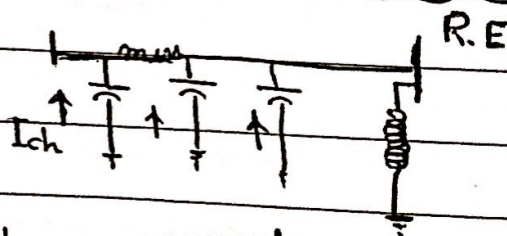
$$C = \frac{1}{2\pi \times 60 \times 433.38} = 6.1 \mu\text{F}$$




$$\text{Reactor constant} = \begin{vmatrix} 1 & 0 \\ y & 0 \end{vmatrix}$$

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{line}} \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{shunt-Reactor}}$$

بیش از ۱۱ میلیون بار

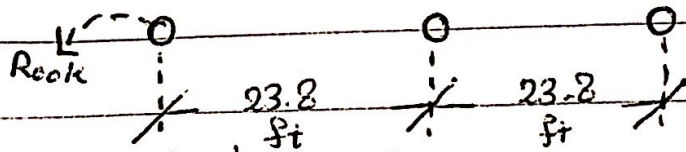* Ex:- (1) A (3 ϕ), 60 Hz, 230 mi Transmission line has
 3 conductors, flat horizontal, spacing is 23.8 ft



the load at the (R-E) is 125 MW at (1 p.f) ~~conductors~~
 and ~~0.25 kV~~ 215 kV

- Find the Voltage Regulation for un-Compensated line.
- A shunt Reactor is Connected at the (R-E) during no-load Condition if the reactor Compensates 70% of the total line admittance, Calculate the Voltage Regulation of the Compensated line?

solution

A) $\gamma L = (\sqrt{ZY}) l$

$$Z = r + jX_L = r + j(X_a + X_d)$$

$$GMD = \sqrt[3]{(23.8)(23.8)(47.6)} = 30.15 \text{ ft}$$

$$A = \cosh(\gamma l) = D$$

$$B = Z_c \sinh(\gamma l)$$

$$V_S = A V_R + B I_R$$

$$C = \frac{1}{Z_c} \sinh(\gamma l)$$


$$\text{Regulation \%} = \frac{\left| \frac{V_S}{A} \right| - V_R}{V_R} \times 100\% = 24.7\%$$

B) $Y_{\text{reactor}} = 0.7 Y_{\text{line}}$

$$Y_{\text{line}} = y \cdot l = 0.001174 \text{ S}$$


$$Y_{\text{reactor}} = \left(\frac{70}{100} \right) (0.001174) = 0.000822 \text{ S}$$
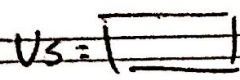
$$\begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{eq}} = \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{\text{lin}} \begin{pmatrix} 1 & 0 \\ -j0.000822 & 1 \end{pmatrix}_{\text{reactor shunt}}$$




$$V_R \% = \frac{\left| \frac{V_s}{A} \right| - V_R}{V_R} \times 100\% = 6.67\%$$

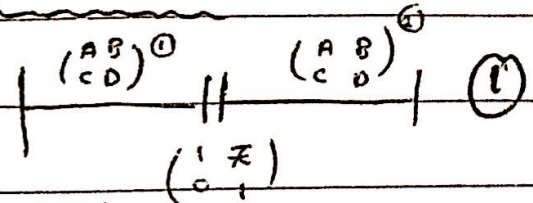Capacitor = $\begin{pmatrix} 1 & Z \\ 0 & 1 \end{pmatrix}$
 Reactance



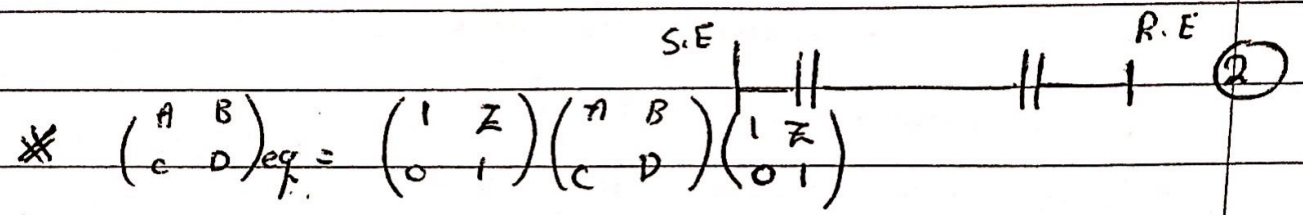
$$\# \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{eq} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} 1 & Z \\ 0 & 1 \end{pmatrix} \begin{pmatrix} A & B \\ C & D \end{pmatrix}$$



$$\# \begin{pmatrix} A & B \\ C & D \end{pmatrix}_{eq} = \begin{pmatrix} 1 & Z \\ 0 & 1 \end{pmatrix} \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} 1 & Z \\ 0 & 1 \end{pmatrix}$$

* Ex 2: Problem (5-15) sadat H.W (4) *

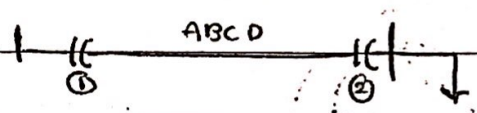

$X_{ct} = 100 \Omega$

$\rightarrow X_{C1} = -j50 \Omega$
 $\rightarrow X_{C2} = -j50 \Omega$

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix}_{eq} = \begin{pmatrix} 1 & -j50 \\ 0 & 1 \end{pmatrix} \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} 1 & -j50 \\ 0 & 1 \end{pmatrix}$$

2015 / 6 / 4

* underground Cables :-

C (overhead line) << C (cable)

لأن GMD في (OHL) كبيرة جداً بينما GMD في (Cable) صغيرة

$$Z_c (\text{cable}) \approx \frac{1}{10} Z_c (\text{OHL})$$

وكذلك نستعملها في الأماكن التي هنقر فيها OHL

OHL

الاستخدام :-

هنا ناحية فنية

Trans

نوصل كما في


الشكل بالشكل

underground

في حفرة

الحجم

1
~ 2.5 cm

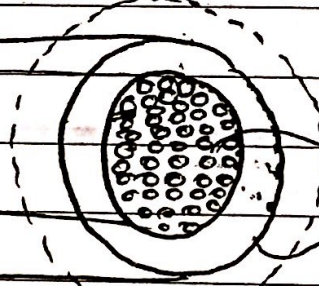

strand conductor

insulation (PVC rubber)

external Protection

PVC Anti chemical

All Cable have :-

- ① Conductor :- Copper or Aluminum.
- ② insulation :-
- ③ external Protection (Anti mechanical Damage)
- ④ PVC (Anti Chemical)

* Ex :-

19 / 0.1

* strand

diam of each strand

(3/20) AWG

American wire Gubh.

(NOTE BOOK)

insulation material :-

requirements of insulation materials.

- 1) very high insulating Resistance (MΩ).
- 2) high dielectric strength. ← *مقاومة عزل كهربائي*
على لأرض ومن عند بيوتها
- 3) good mechanical properties.
- 4) immunity to Chemical attack.
- 5) non-hygroscopic.
- 6) not too cost.


* insulation material type :-

- impregnated paper
- rubber
- PVC
- XLPE ← *مستخرج من مادة البولي إيثيلين*

* (rubber + sulphur) :- vulcanized rubber *خامات عازلة*

* (XLPE) :- Cross-Linked polythene. $(250^{\circ}\text{C} - 300^{\circ}\text{C})$

* insulation Resistance of a Cable :-

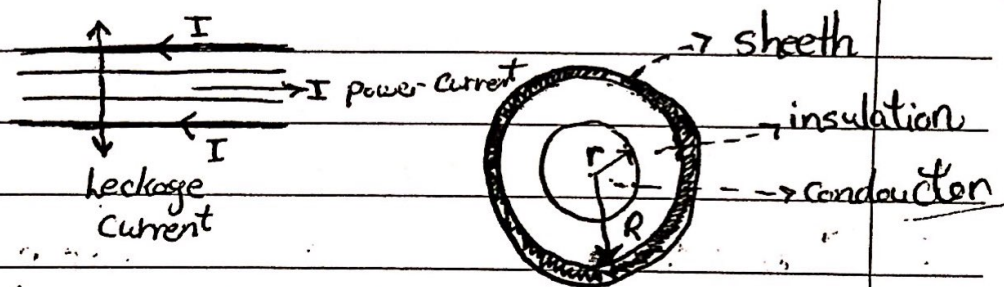

$$dR_{(\text{insulation})} = \rho \frac{dx}{A}, \quad \rho = \text{specific resistance of dielectric}$$

$A = 2\pi(x) \cdot l$: $l = \text{length of current path}$

$l = \Delta x = dx$: $A = \text{Cross section Area normal to flow of Leakage Current}$

$$dR = \rho \frac{dx}{2\pi(x) \cdot l}$$

$$R_{\text{insulation}} = \frac{\rho}{2\pi} \int_r^R \frac{dx}{x} = \frac{\rho}{2\pi} \ln \frac{R}{r}$$

for l (m)

$$R_{\text{ins}} = \frac{\rho}{2\pi l} \ln \frac{R}{r} \rightarrow * (\Omega)$$

* Ex:- A single core cable (1 core cable).
has core diam of 2.5 cm insulation
thickness of 1.25 cm.

$$\rho = 4.5 \times 10^{14} \Omega\text{-cm}$$

calculate R_{ins}/km ?


Solution

$$R = \frac{\rho}{2\pi l} \ln \frac{R}{r} = \frac{4.5 \times 10^{14} \Omega\text{-cm}}{2\pi (10^5 \text{ cm})} \ln \left(\frac{\left(\frac{2.5}{2}\right) + 1.25}{1.25} \right)$$


\nwarrow
 \swarrow
1 km

$$R_{\text{ins}} = 496 \text{ M}\Omega$$

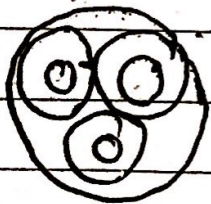* Capacitance of single Core Cable:- 2015/6/8




3- core
Cable

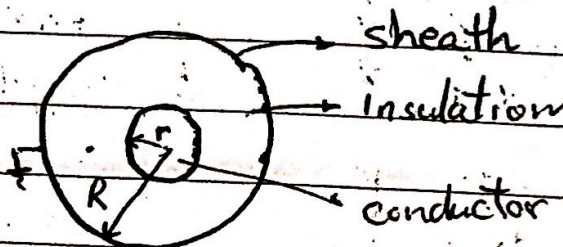

1- single
core

$$E_x = \frac{Q}{2\pi\epsilon x}$$
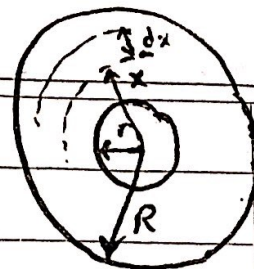
$$V/m, \quad \epsilon = \epsilon_0 \epsilon_r \rightarrow \text{①}$$



ϵ = permittivity of insulation material

E_x = Electric field intensity

$$V = \int_r^R E_x dx = \text{Voltage Conductor (w.r.t) sheath.}$$

$$V = \int_r^R \frac{Q}{2\pi\epsilon x} = \frac{Q}{2\pi\epsilon_0 \epsilon_r} \ln \frac{R}{r} \rightarrow \text{②}$$

$$C = \frac{Q}{V} = \frac{2\pi\epsilon_0 \epsilon_r}{\ln(\frac{R}{r})} \text{ f/m} = \frac{0.0556 \epsilon_r}{\ln(\frac{R}{r})} \mu\text{f/km}$$

Capacitance (cable) $\gg \gg$ Capacitance (over head line)


I_{ch} (cable) \gg I_{ch} (over head line)

② For ① $\rightarrow Q =$:-

$$E_x = \frac{V \cdot 2\pi\epsilon_0 \epsilon_r}{\ln(\frac{R}{r})} \cdot \frac{1}{2\pi\epsilon_0 \epsilon_r x}$$

$$E_x = \frac{V}{x \ln(\frac{R}{r})}$$
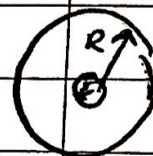
$$* E_{max} = \frac{V}{r \ln(\frac{R}{r})} \quad \text{①}$$



$$* E_{min} = \frac{V}{R \ln(\frac{R}{r})} \quad \text{②}$$

The min value of (E_{max}) at the surface of the Conductor is when

$$\frac{\partial E_{max}}{\partial r} = 0 = 0 - \frac{V [\ln(\frac{R}{r}) - 1]}{(r \ln(\frac{R}{r}))^2} = 0$$

$$= - \frac{V}{(r \ln(\frac{R}{r}))^2} (\ln(\frac{R}{r}) - 1) = 0$$

$$\ln(\frac{R}{r}) = 1 \quad \frac{R}{r} = e^1 = 2.718$$

$$R = r (2.718)$$

* Ex :- (1)

Determine the most economic diameter of a (1-core) cable, metal sheathed the working voltage is (85 kv), And the ~~elect~~ dielectric strength of the insulating material is (65 kv/cm)

for economic size, $\frac{R}{r} = 2.718$

$$V = E_{max} r \ln\left(\frac{R}{r}\right)$$

$E_{max} \leq$ dielectric strength

$$85 = 65 (r) (1)$$

$$r = \frac{85}{65} = 1.3 \text{ cm}$$

$$\text{cond. diameter} = 2(r) = 2(1.3) = 2.6 \text{ cm}$$

$$\text{sheath diameter} = 2.718 \times 2 \times 1.3 = 7.07 \text{ cm}$$

* Ex :- (2)

Calculate the Capacitance And charge current of a single Core Cable used on 66 kv supply, 3-ph 50-Hz system.

the Cable is (1 km) long

core diameter (15 cm) sheath

diameter (60 cm), $G_r = (3.6)$

3 single Core






3-Ph

$$C_n = \frac{0.0556 G_r}{\ln \frac{R}{r}} = \frac{0.0556 \times 3.6}{\ln \left(\frac{60/2}{15/2} \right)} = 0.145 \mu\text{f}/\text{km}$$

$$I_{ch} = \omega C_n V_{ph}$$

$$= 2\pi \times 50 \times 0.145 \times 10^{-6} \times \left(\frac{66 \times 10^3}{\sqrt{3}} \right) = 1.74 \text{ A}/\text{km}$$

* Capacitance of 3-core belted cables:-

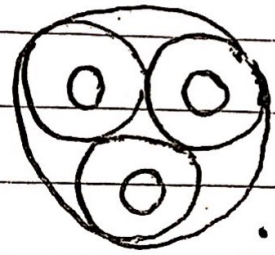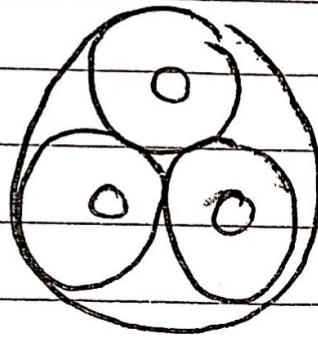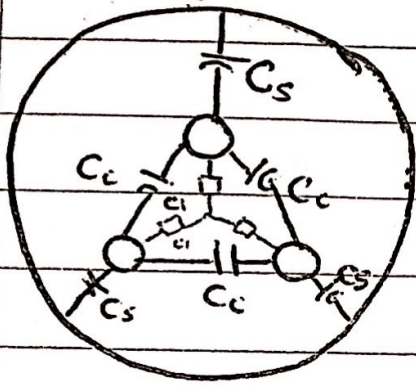

using (Δ -Y) transfer:-

$$Z_Y = \frac{1}{3} Z_{\Delta}$$

$$\frac{1}{Y_{C1}} = \frac{1}{3} \cdot \frac{1}{Y_{C_c}}$$


$$C_1 = 3C_c$$

if the neutral point is at zero potential, And sheath is also at zero poten

$$C_1 \parallel C_s$$

$$C_0 = C_1 + C_s$$

$$C_0 = 3C_c + C_s$$

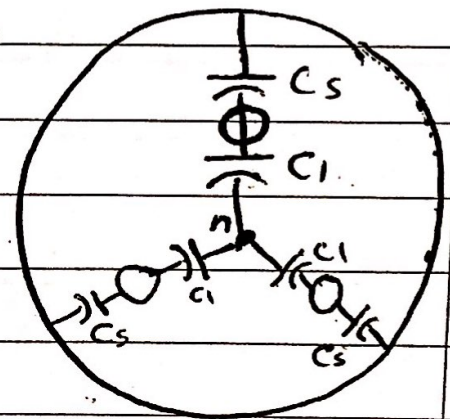

$$C_0 = \frac{3}{2} C_a - \frac{C_b}{6}$$

2015 / 6 / 11

Ex:-

3-Ph, 3-core, metal sheathed cable gave following results on test:

- i) Cap between bunched conductors & sheath is $0.625 \mu\text{f}/\text{km}$.
- ii) Cap between two conductors bunched with sheath & third conductor is $0.4 \mu\text{f}/\text{km}$.

Determine

- a) the cap between any two conductors.
- b) the cap between any two bunched conductors.
- c) the charging current /Ph/km when the cable is connected to 10 kv, 50Hz supply.

solution



a)

$$C_b = 0.625 \mu\text{f}/\text{km} = 3C_s \quad C_s = \frac{0.625 \mu\text{f}/\text{km}}{3}$$

$$C_s = 0.20833 \mu\text{f}/\text{km}$$

$$C_a = 0.4 = 2C_c + C_s$$
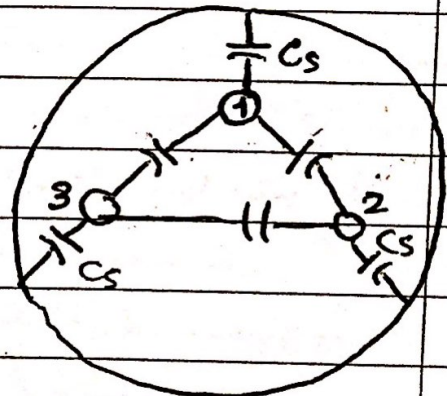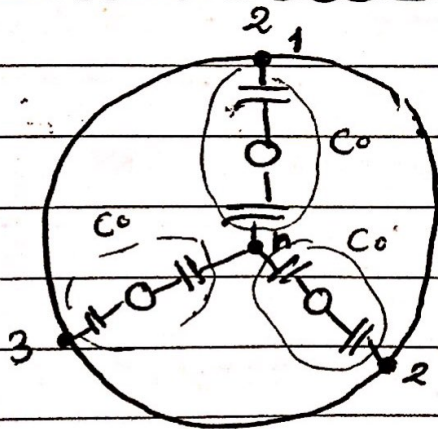
$$C_c = \frac{0.4 - 0.20833}{2} = 0.0958 \mu\text{f}/\text{km}$$





$$C_0 = 2C_c + C_s$$


$$(neutral) = 2(0.0958) + (0.20833) = 0.496 \mu\text{f}/\text{km}$$

$$C_{12} = \frac{C_0 \times C_0}{(C_0 + C_0)} =$$
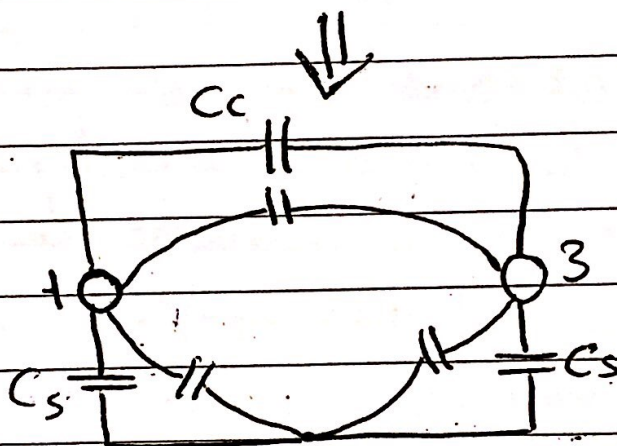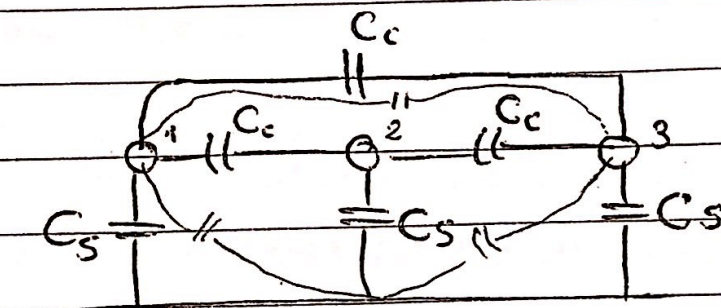
$$\frac{C_0^2}{2C_0} = \frac{C_0}{2} = \frac{0.496}{2} = 0.248 \mu\text{f/km}$$



b)

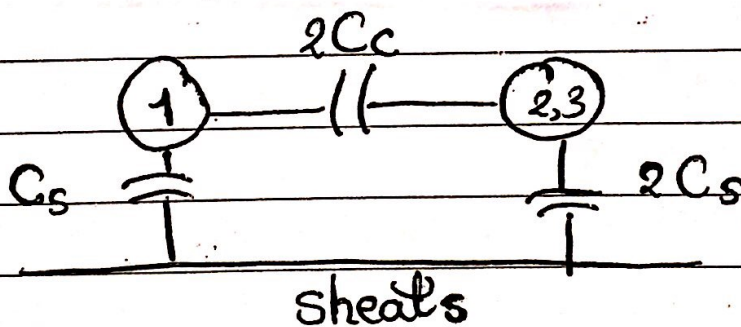

$$C_{23,1} = 2C_c + \frac{C_s \cdot 2C_s}{(C_s + 2C_s)} = 2C_c + \frac{2C_s}{3}$$

$$C_{23,1} = 2(0.0958) + \frac{2}{3}(0.20833) = 0.33 \mu\text{f/km}$$

c) $I_{ch} = W C_o V_p$

$$= \frac{2\pi (50) (0.496 \times 10^{-9}) \times 10000}{\sqrt{3}} = 0.899 \text{ A/km}$$

* EX:- # (2)

A single core (1-core), cable of (5 km) long has a conductor diam of (2 cm), inside diam of sheath of (5 cm). the cable is used at ~~49.9~~ 24.9 kV & 60 Hz. Calculate :-

- (max) & (min) electric stress.
- optimum value of conductor radius that gives min value of max. stress.

solution


$$E_{max} = \frac{V}{r \ln \frac{R}{r}} = \frac{24.9}{1 \ln \left(\frac{2.5}{1} \right)} = 27.17 \text{ kv/cm}$$

$$E_{min} = \frac{24.9}{2.5 \ln \frac{2.5}{1}} = 10.87 \text{ kv/cm}$$


$$r = \frac{R}{2.718} = \frac{2.5}{2.718} = 0.92 \text{ cm}$$

$$\text{min value of max stress} = \frac{24.9}{0.92 \ln \frac{2.5}{0.92}} = 27.07 \text{ kv/cm}$$

heating of Cables :-

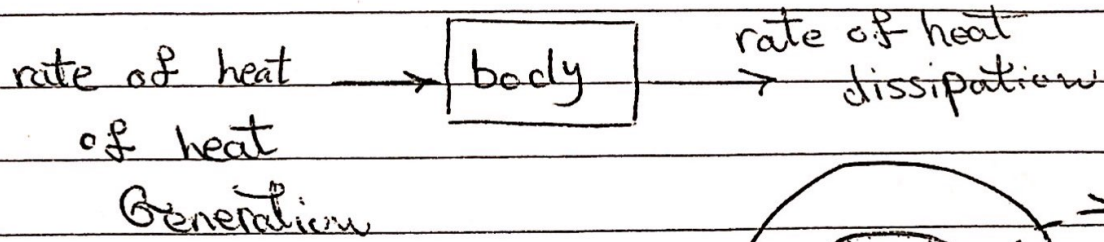


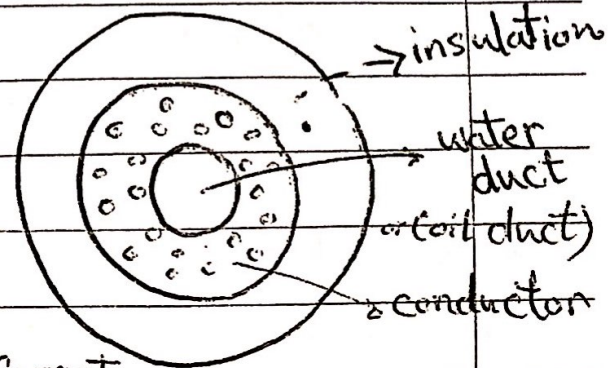Sources of heat generation is underground cables :-




1) Core loss : $I^2 R$, I : Load Current carried by the cable.

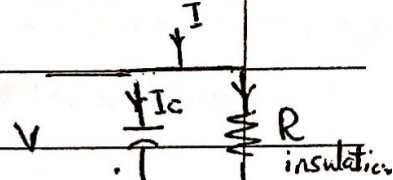2) dielectric loss : (a) Power loss due to the flow of leakage current through ($R_{insulation}$).



(b) Hysteresis losses

3) sheath loss

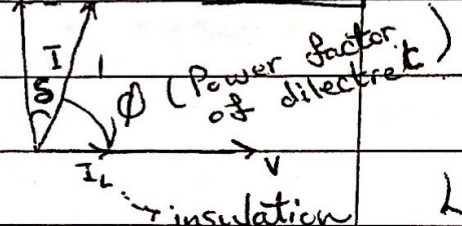

Total loss dielec = hysteresis loss

+ Power due to the flow leakage current through (R_{insul})

hyster \rightarrow Power dielec flow

$\cos \phi$ = Power factor of die

$\sin \delta$ = " " "

dielec Power loss = $V I \cos \phi$

" " = $V I (\sin \delta)$

" " = $V (WC V) \delta$

" " = $WC V^2 \delta$

Ex: # ①

A single-core cable has a conductor diam of (0.814 in), inside diam of sheath of (2.442 in) and a length of (3.5 mi). The cable is operated at (60 Hz), (7.2 kV). The dielectric constant is (3.5) and the (P.F.) of the dielectric on open circuit at rated (P.F.) $\epsilon(V)$ is (0.03). The insulation resistivity is $(1.3 \times 10^7 \text{ M}\Omega/\text{cm})$.

Calculate:-

- (Max) stress in the dielectric
- cap of the cable
- charging current
- insulation resistor
- Power loss due to leakage current through (R_{insulation})
- hyst. loss
- total dielectric loss

Solution

$$r = \frac{0.814}{2} \times 2.54 = 1.03 \text{ cm}$$

$$R = \frac{2.442}{2} \times 2.54 = 3.1 \text{ cm}$$

$$a) E_{\max} = \frac{V}{r \ln \frac{R}{r}} = \frac{7200}{1.03 \ln \left(\frac{3.1}{1.03} \right)} = 6.34 \text{ kV/cm}$$

$$b) C = \frac{0.0556 \epsilon \text{ cm}}{\ln(R/r)} = \frac{0.0556 (3.5)}{\ln(3.1/1.03)} = 0.18 \frac{\mu\text{F}}{\text{km}} \times 3.5 \times 1.6 = 0.996 \mu\text{F}$$

$$c) I_{ch} = WC.V = (2\pi \times 60)(0.996 \times 10^{-6})(7200) = 2.7 \text{ A}$$

$$d) R_{\text{insulation}} = \frac{\rho}{2\pi l} \ln\left(\frac{R}{r}\right) = \frac{1.3 \times 10^7 \text{ M}\Omega\text{-cm}}{2\pi (3.5 \text{ m} \times 160.9 \times 10^6)} \ln\left(\frac{3.1}{4.03}\right)$$

$$R_{\text{insulation}} = 4 \text{ M}\Omega$$

$$e) P_{\text{loss due to Leakage current}} = \frac{V^2}{R_{\text{insulation}}} = \frac{(7200)^2}{4 \times 10^6} = 12.85 \text{ Watt}$$

$$f) P_{\text{total}} = W C V^2 S \rightarrow \text{rad} \\ = (2\pi 60) (0.996 \times 10^{-6}) (7200)^2 (0.03) = 584 \text{ W}$$

$$g) P_{\text{hyst}} = P_{\text{total}} - P_{\text{insulation}} = 584 \text{ W} - 12.85 \text{ W} = 571.16 \text{ Watt}$$

$$R = \frac{\rho}{2\pi l} \ln \frac{R}{r}$$

$$480 = \frac{\rho}{2\pi l} \ln \frac{2}{1}$$

$$960 = \frac{\rho}{2\pi l} \ln \left(\frac{x + 1.5}{1.5} \right) \text{ W}$$

$$\frac{1}{2} = \frac{\ln 2}{\ln w}$$

$$\ln w = 2 \ln 2$$

$$w = e^{2 \ln 2} = 4$$

$$w = 4 = \frac{1.5 + x}{1.5}$$

$$x = 4.5 \text{ mm}$$